

# Physics 590B


## Electrical signals generation and measurements

**Torpedo nobiliana (Giant electric ray)**

**Typical pulse: 50 A, 60 V**




# Connecting resistors in series

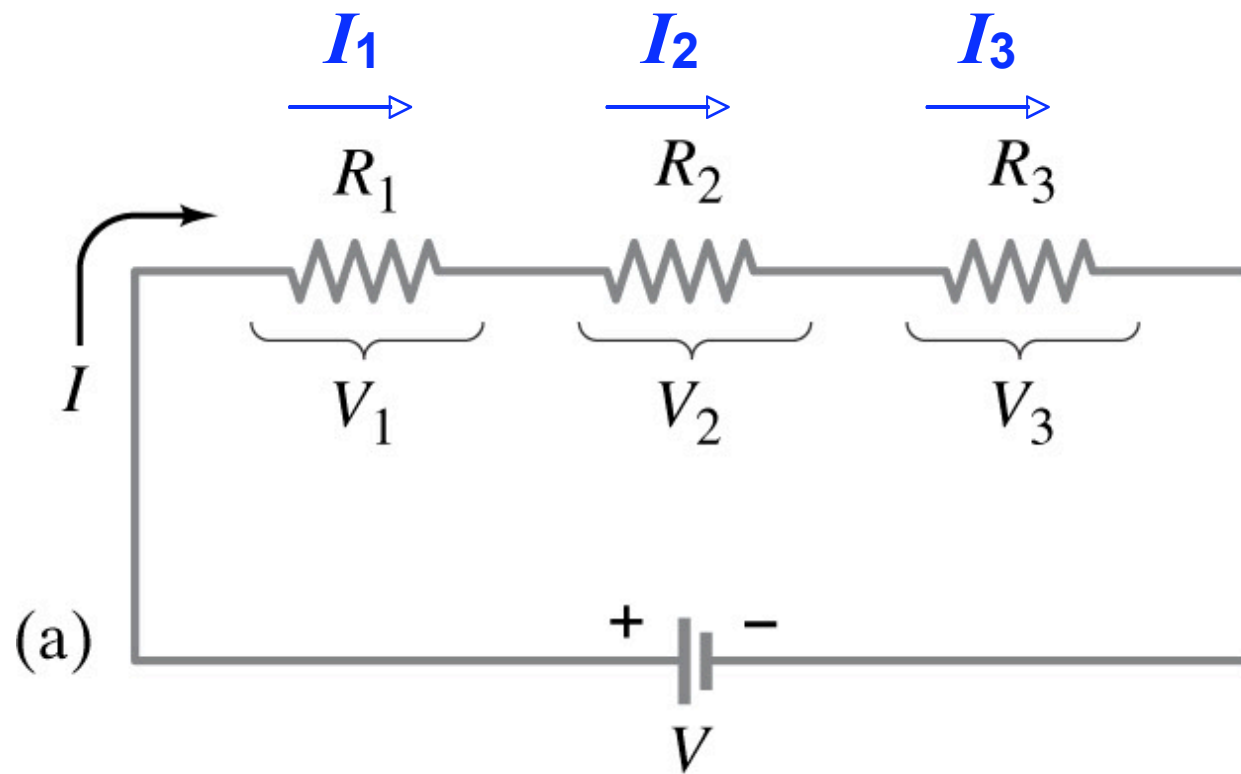

$$I_1 = I_2 = I_3 = I$$

$$V_1 = IR_1 \quad V_2 = IR_2 \quad V_3 = IR_3$$


$$V = V_1 + V_2 + V_3$$

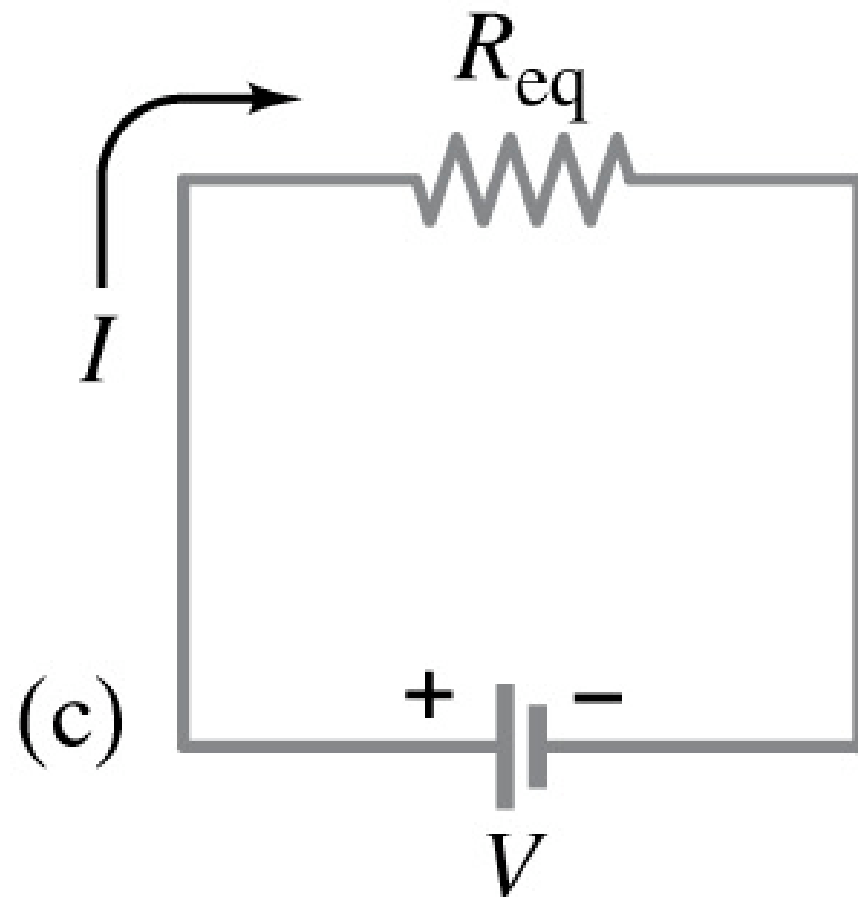

$$V = IR_{eq} \quad (\text{same } I \text{ and } V \text{ as before})$$

$$R_{eq} = R_1 + R_2 + R_3$$


# Connecting resistors in parallel

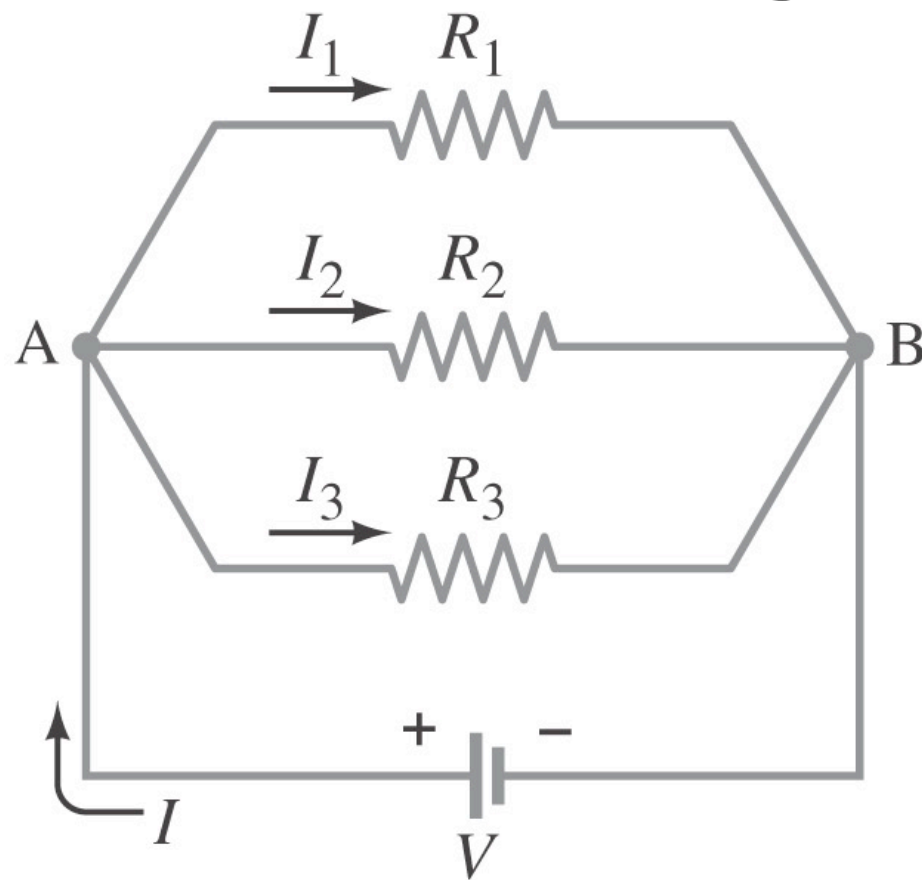

$$I = I_1 + I_2 + I_3$$

$$V = V_1 = V_2 = V_3$$
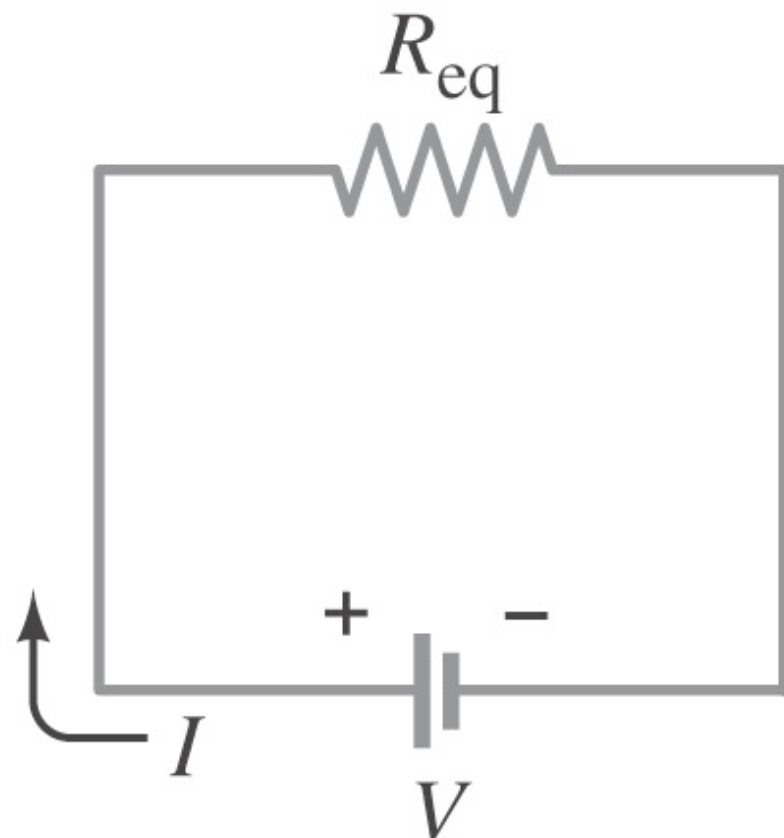
$$V = I_1 R_1 \quad V = I_2 R_2 \quad V = I_3 R_3$$




$$V = IR_{eq} \quad (\text{same } I \text{ and } V \text{ as before})$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


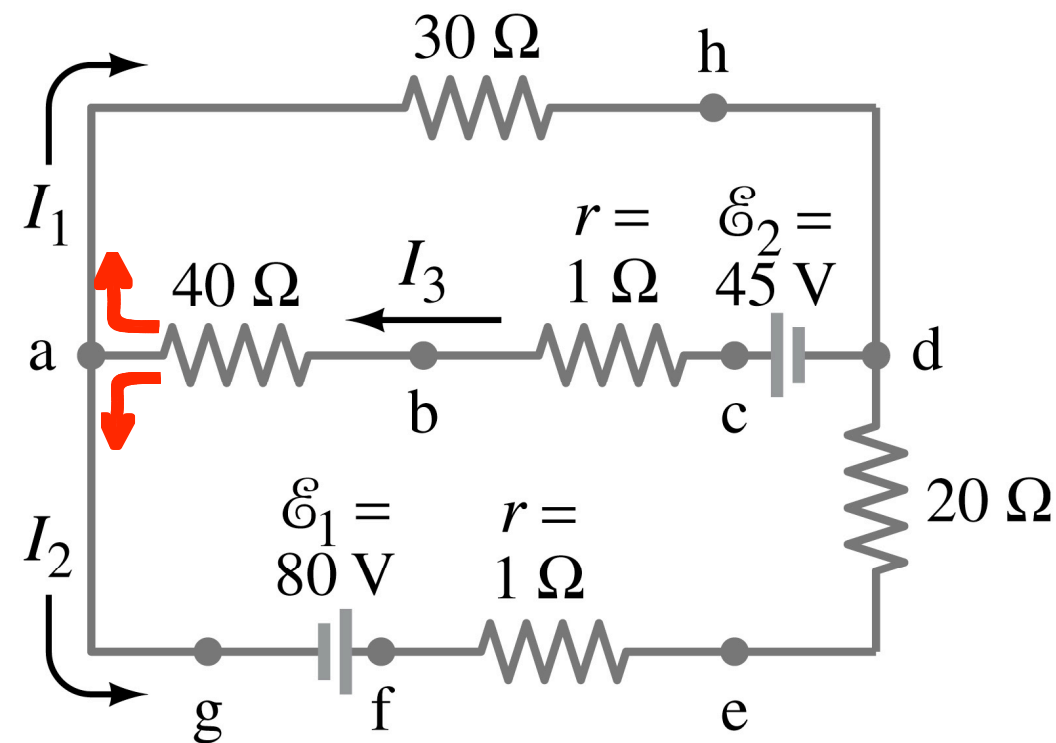
# Kirchhoff's rules

**Junction rule:** Sum of currents entering a junction equals the sum of the currents leaving it.




e.g. at a,  
 $I_3 = I_1 + I_2$

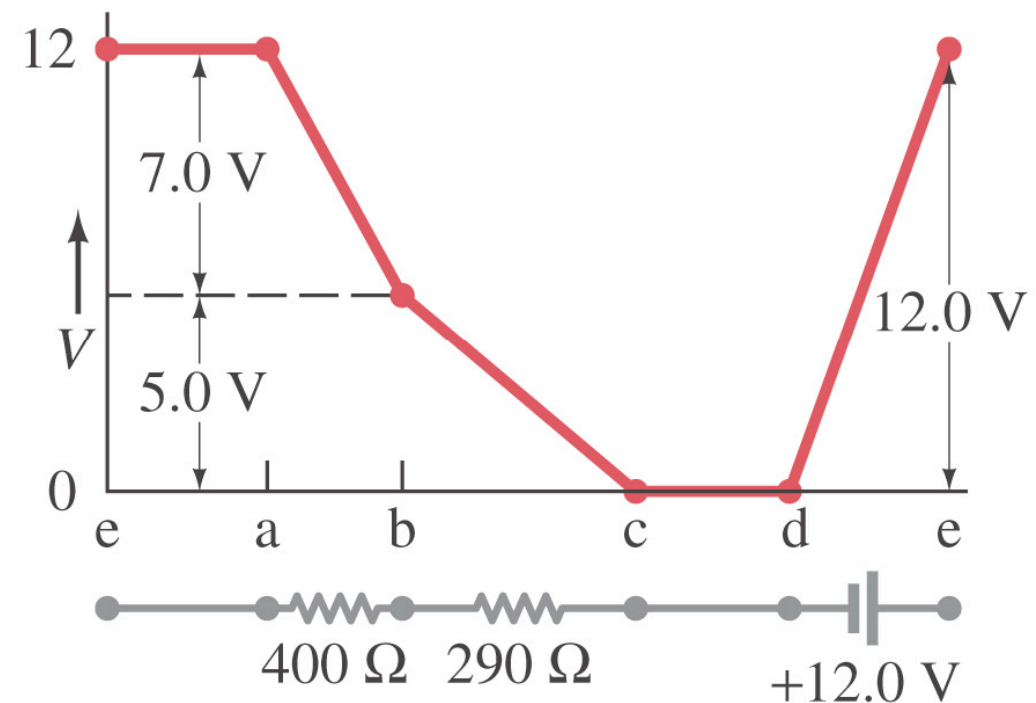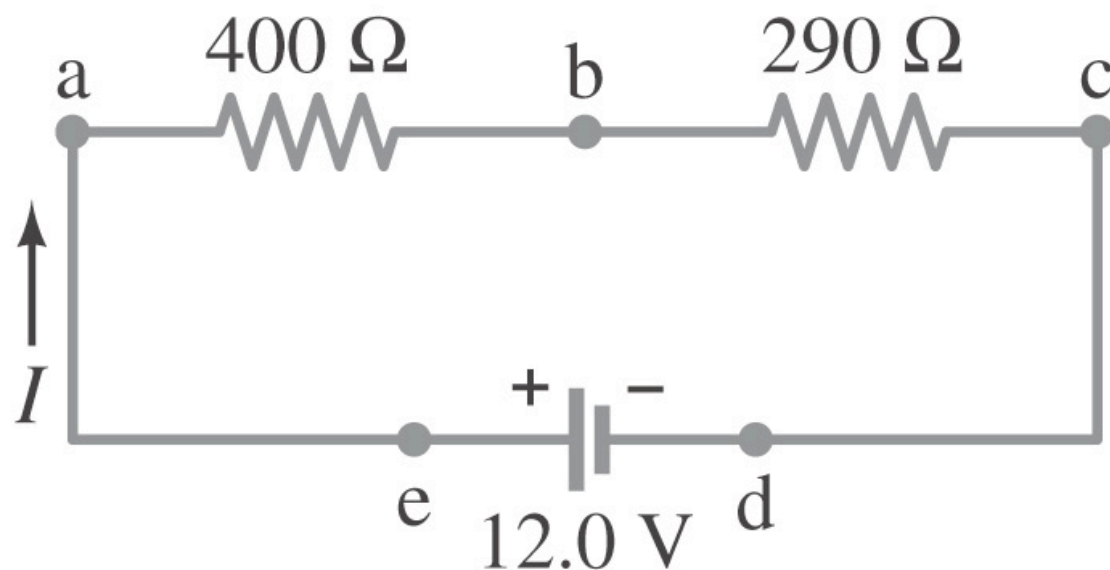
**Loop rule:** The sum of the changes in potential around a closed loop is zero.





# Resistivity measurements

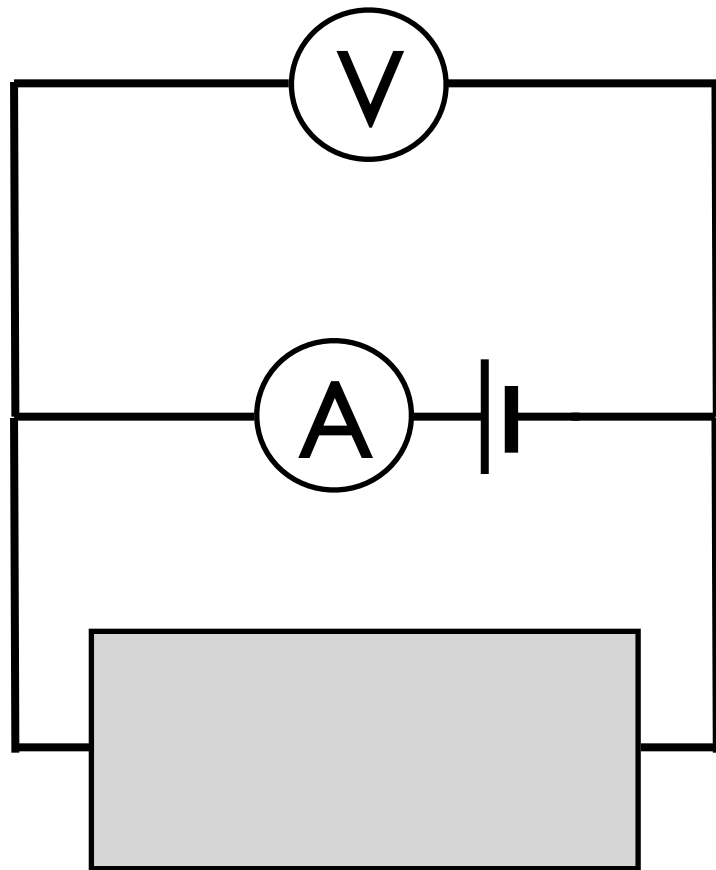



# Resistivity measurements

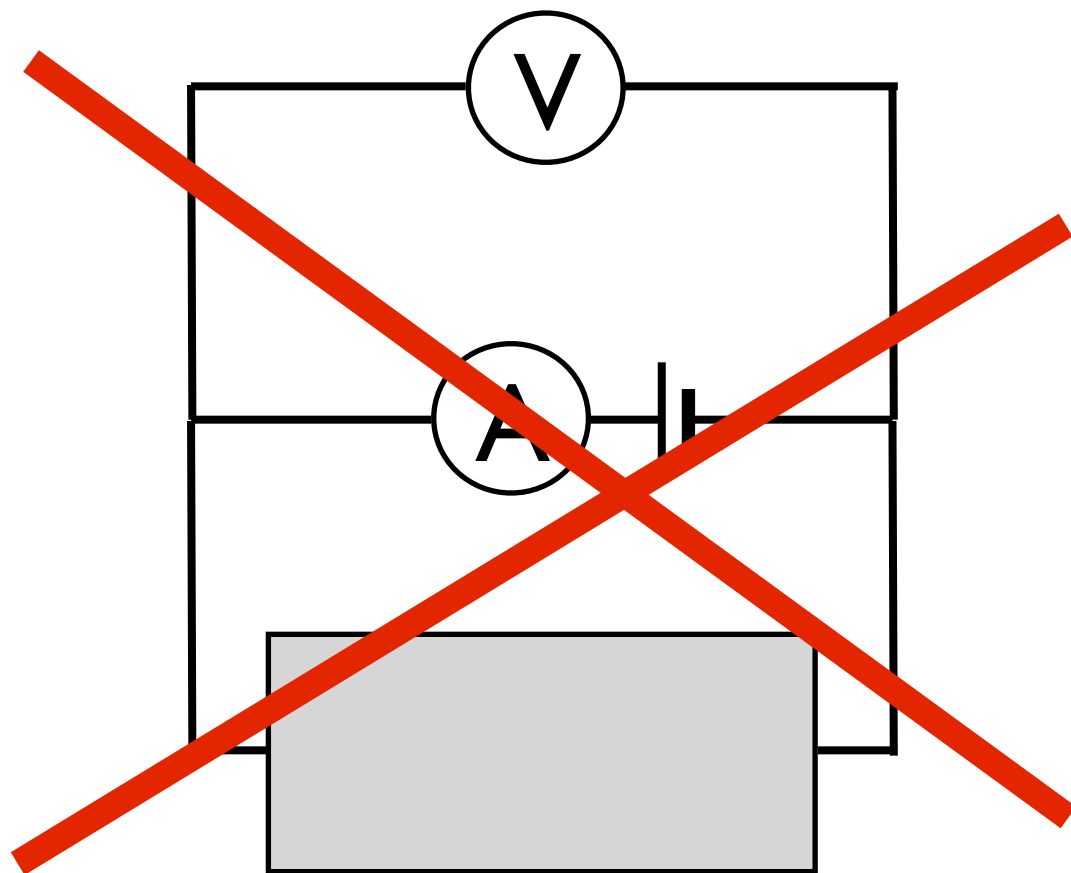

# Resistivity measurements

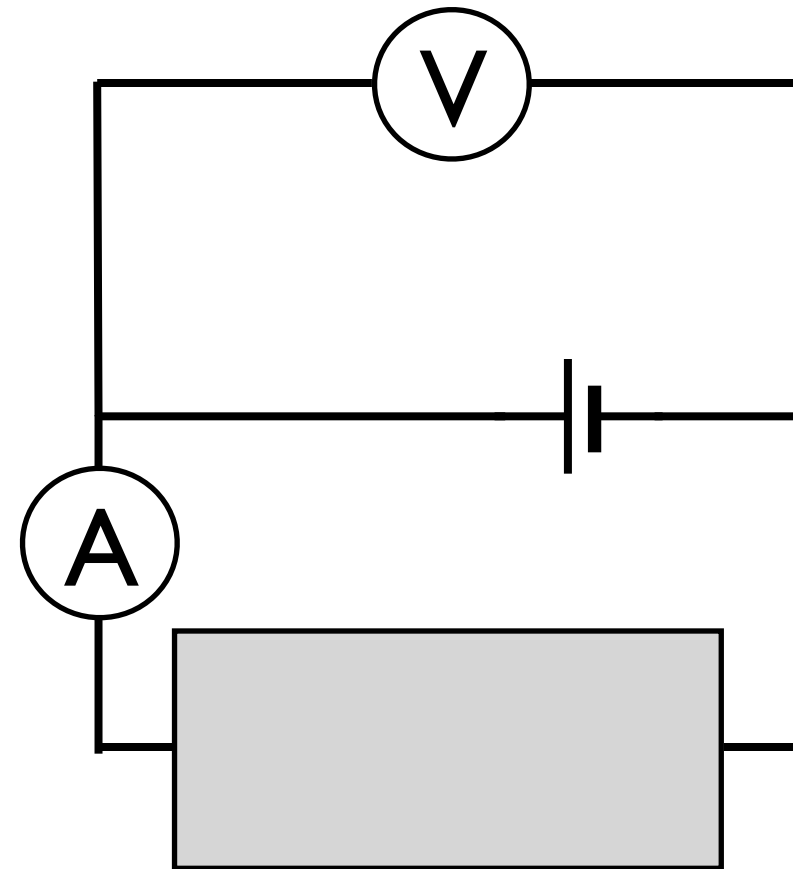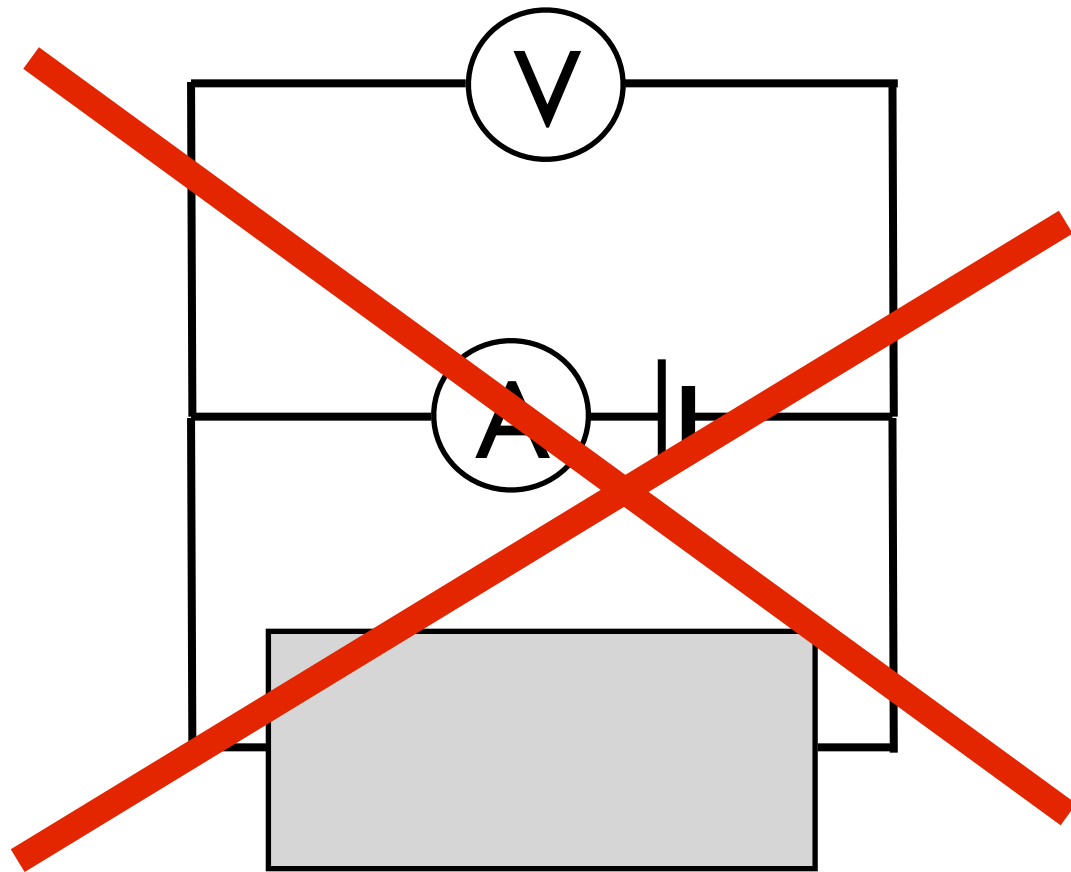


# Resistivity measurements

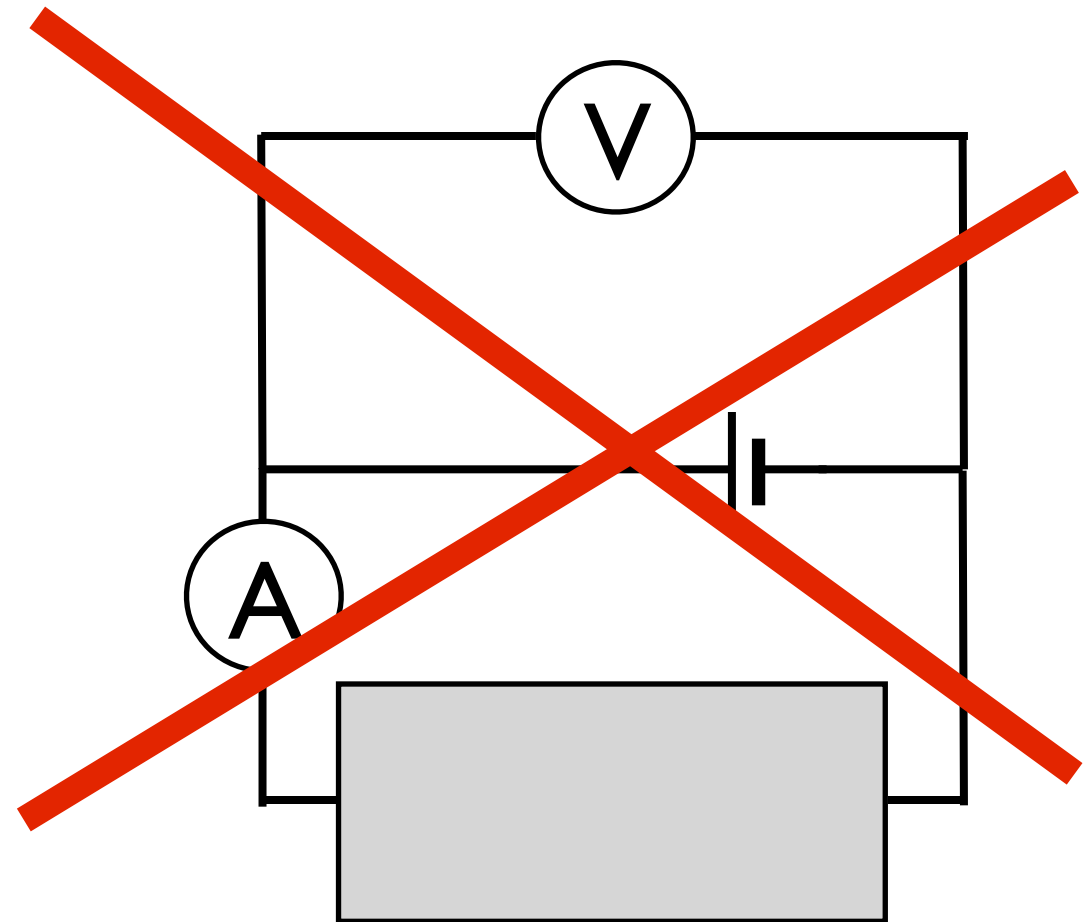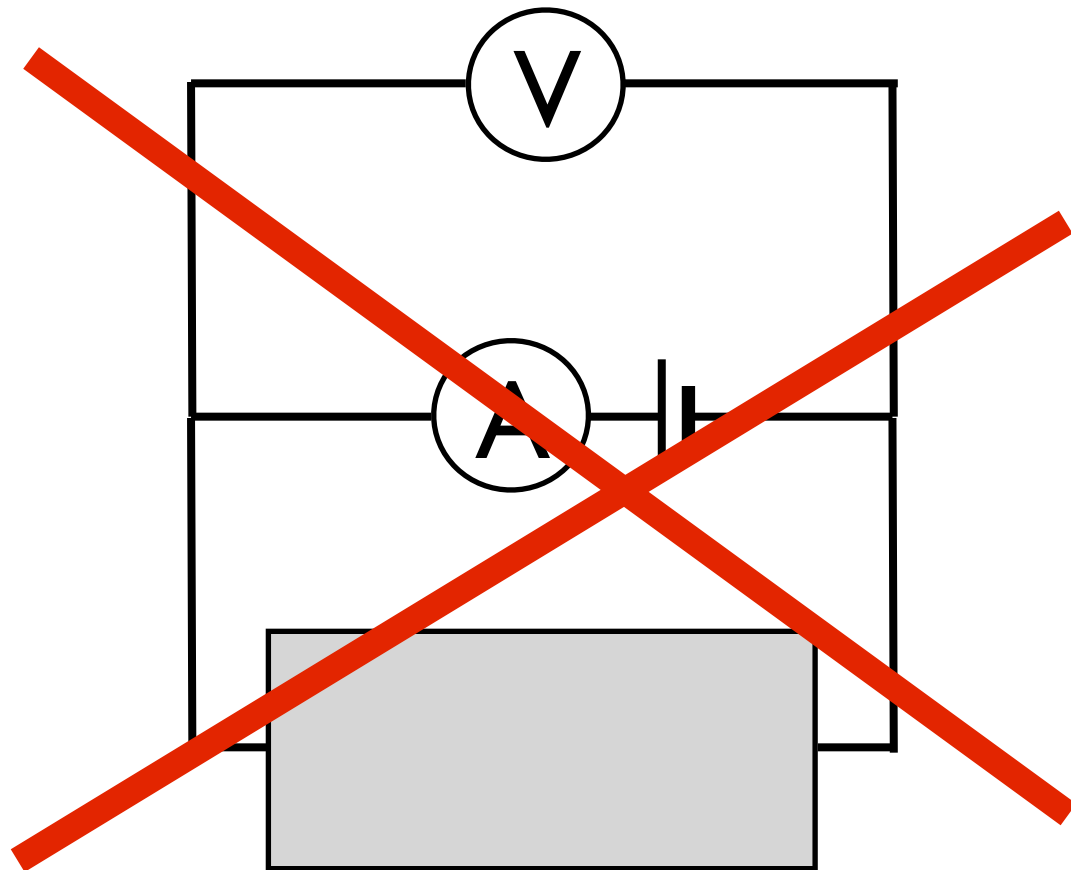






# Real circuit

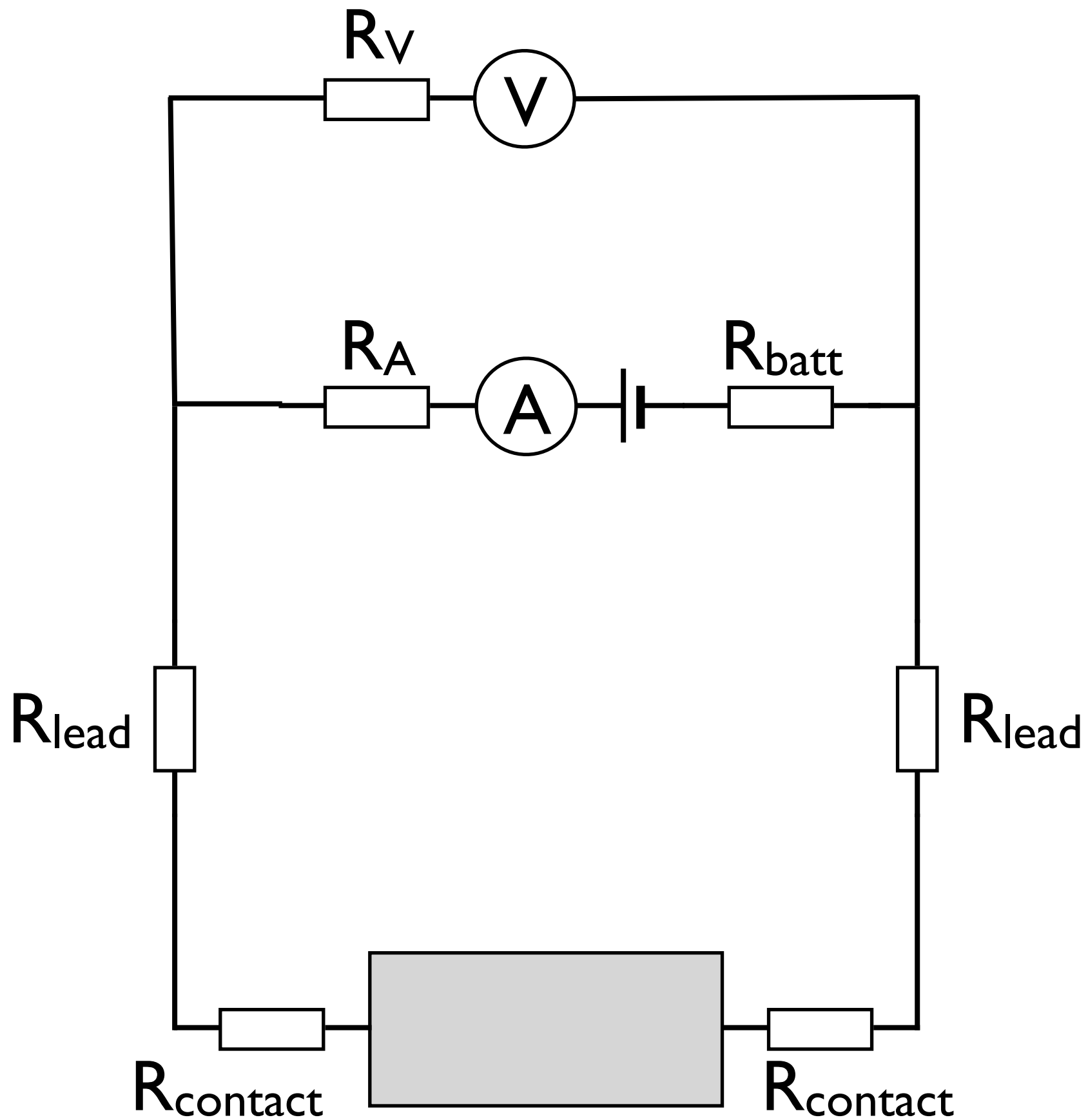

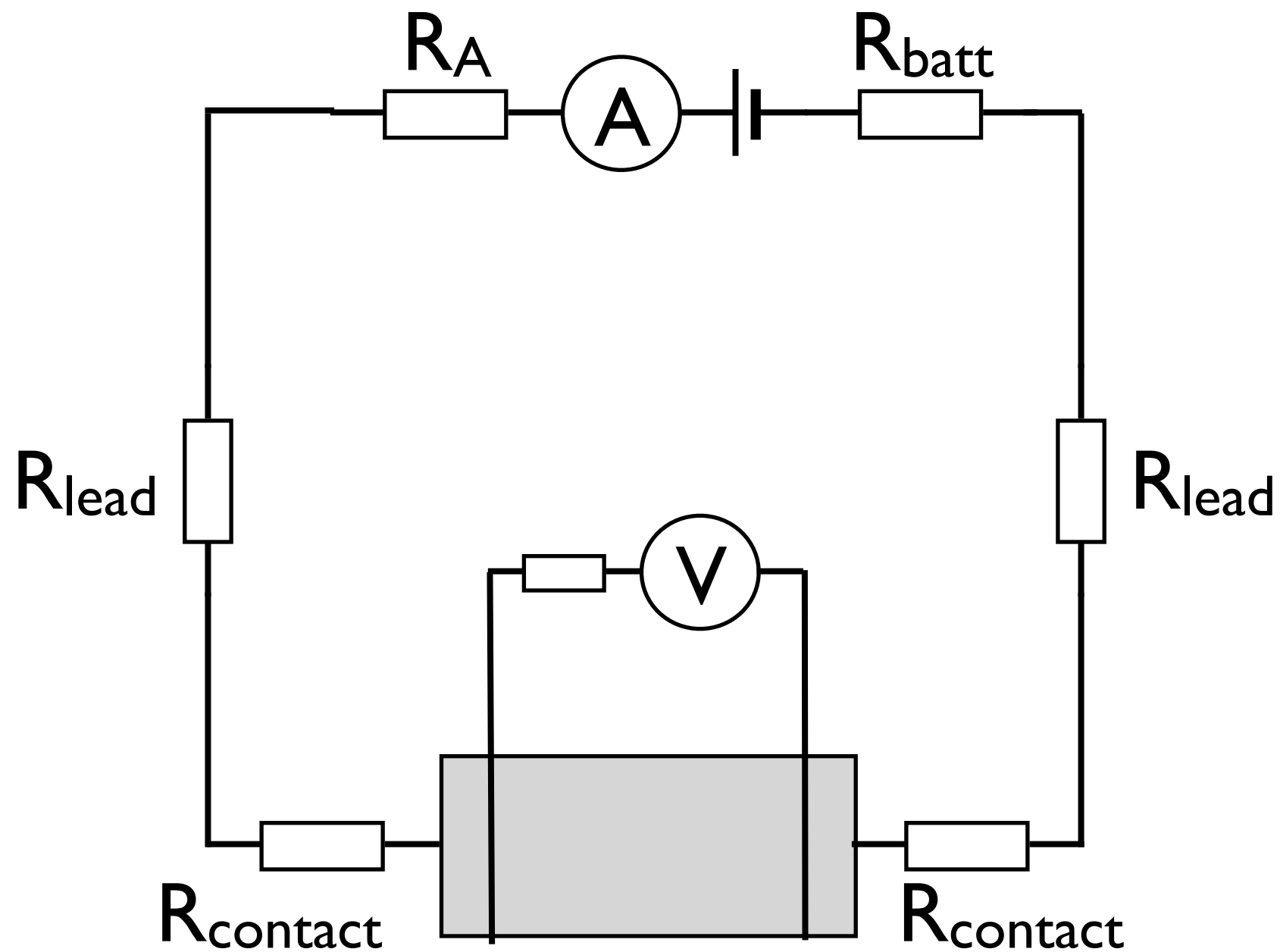
# Solution: four point contact measurement



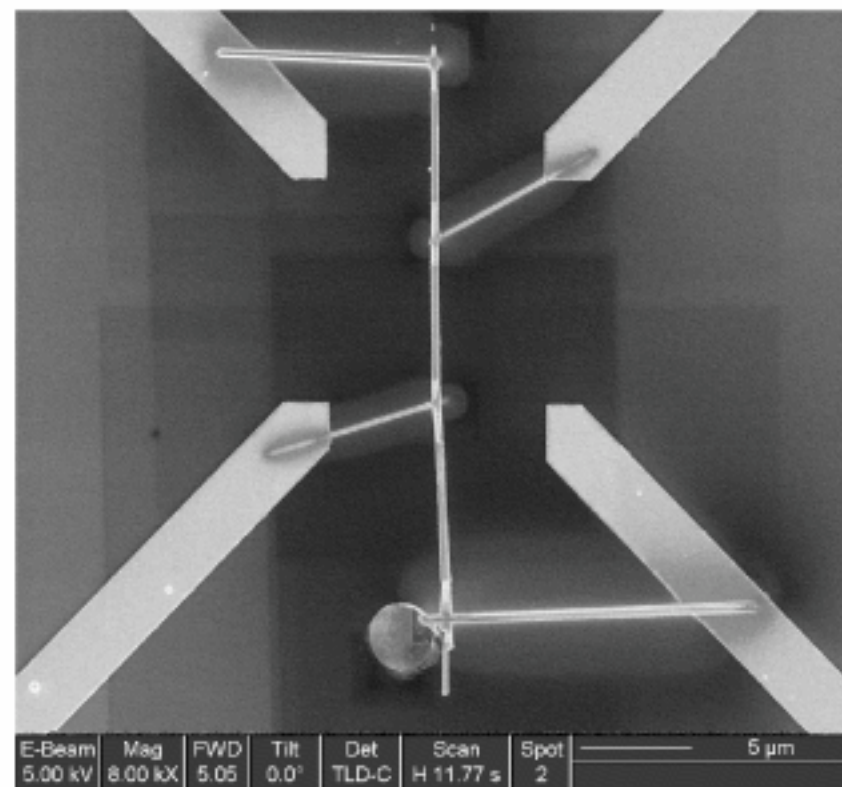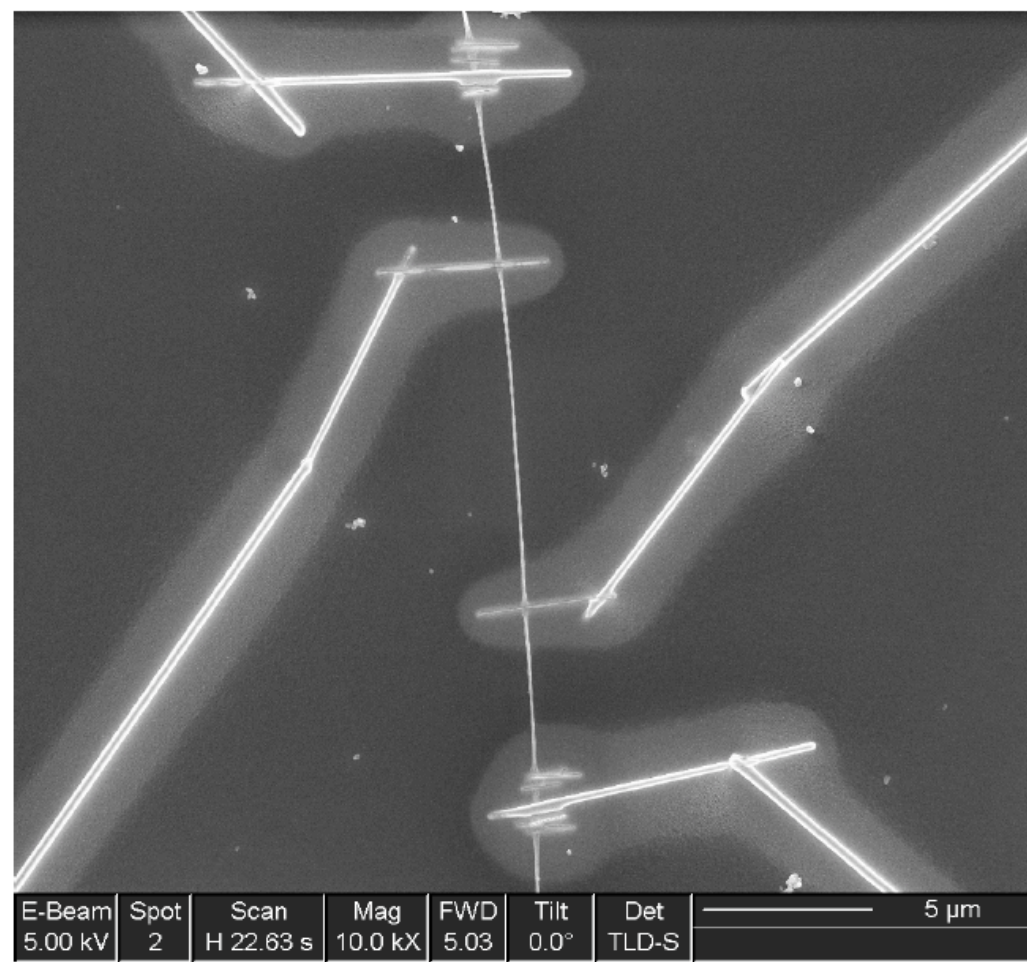


# Simplest circuit: voltage divider





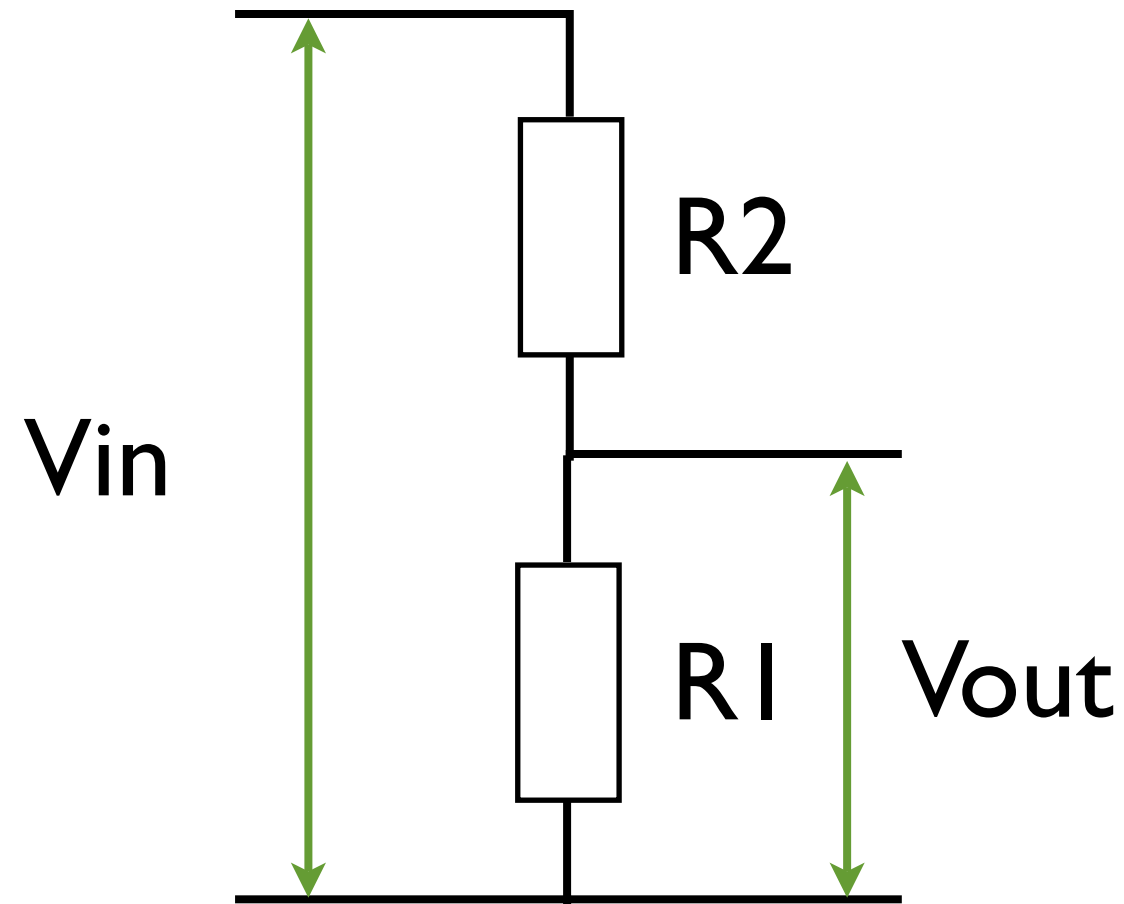


$$V_{out} = V_{in} \frac{R_1}{R_1 + R_2}$$

# Batteries


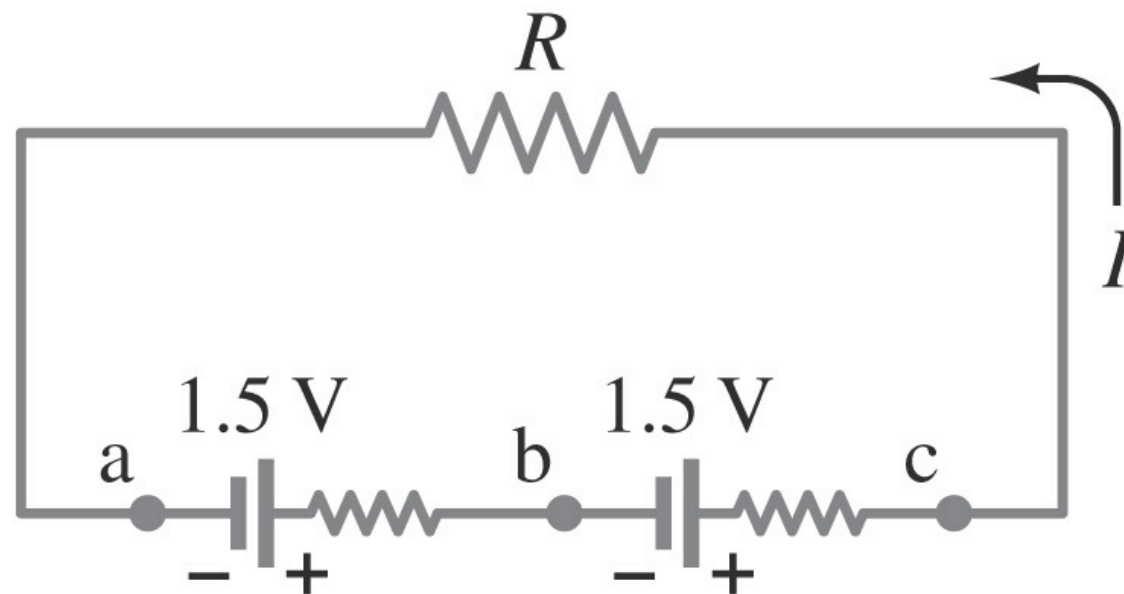


# Analog power supplies

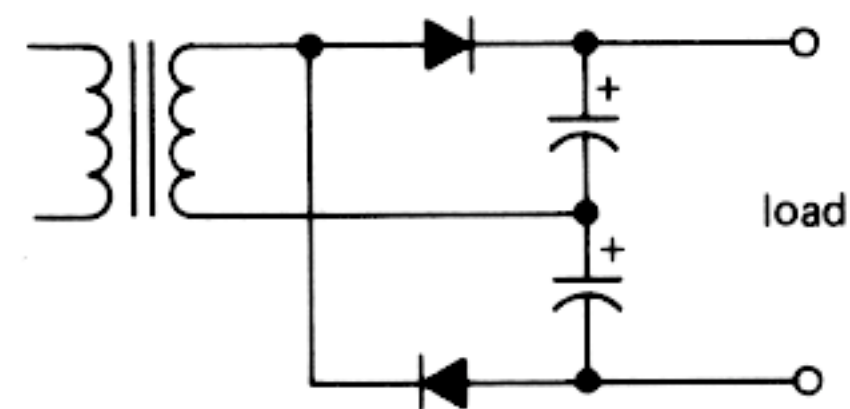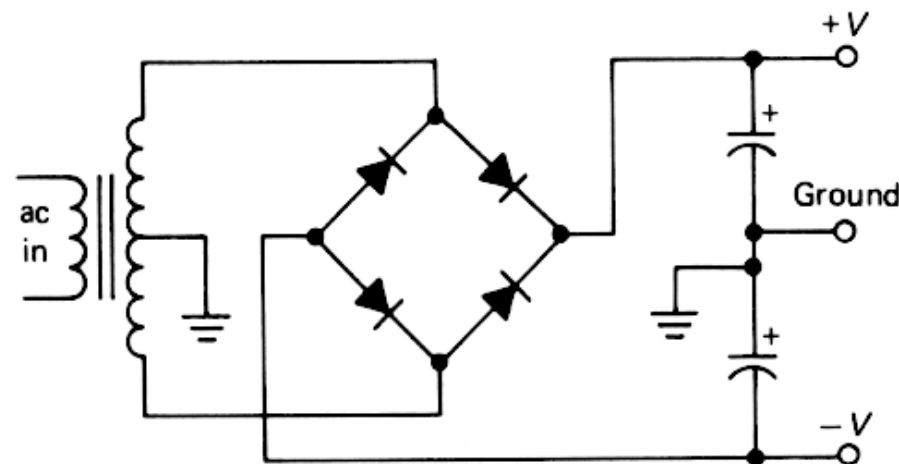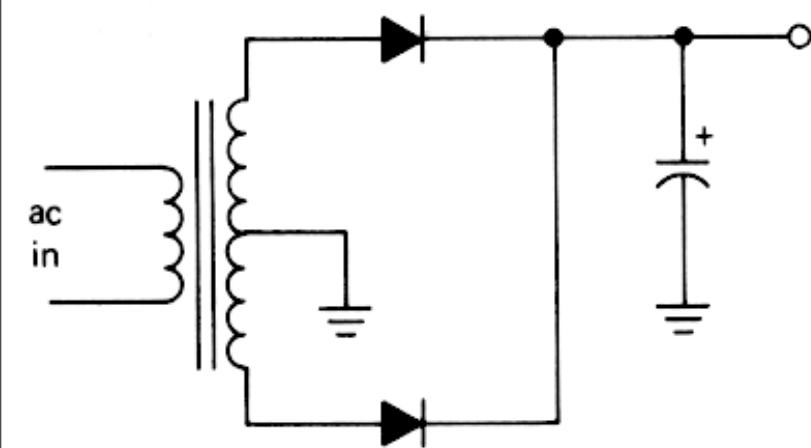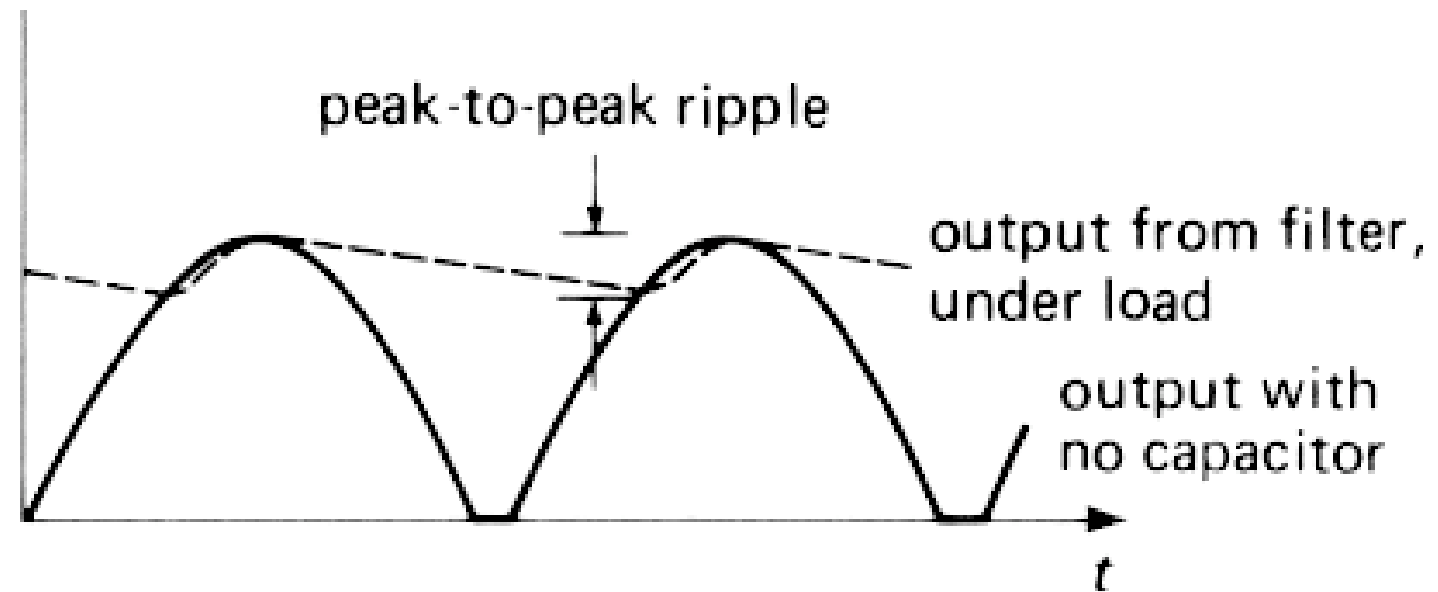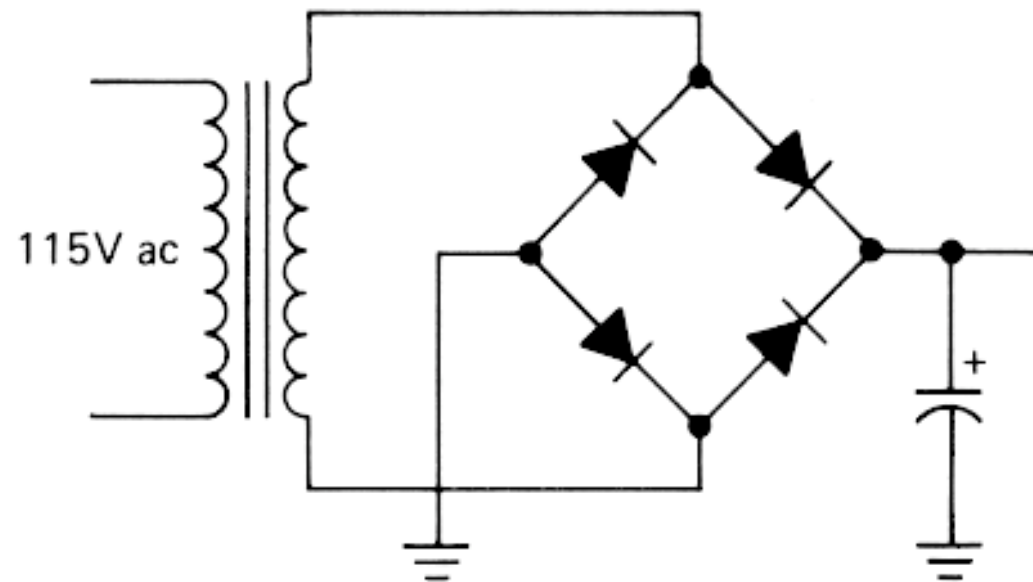


# Voltage regulators

## Block Diagram

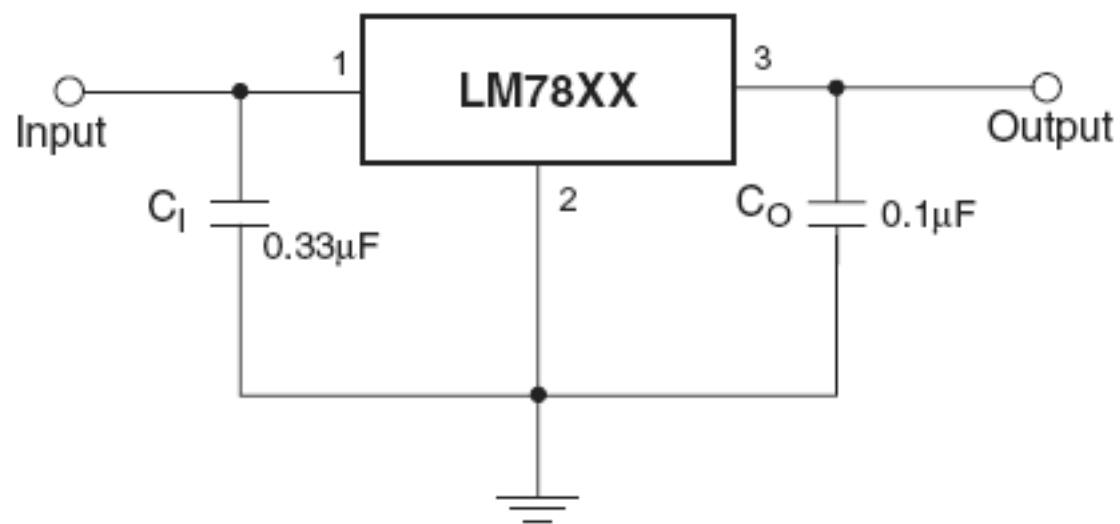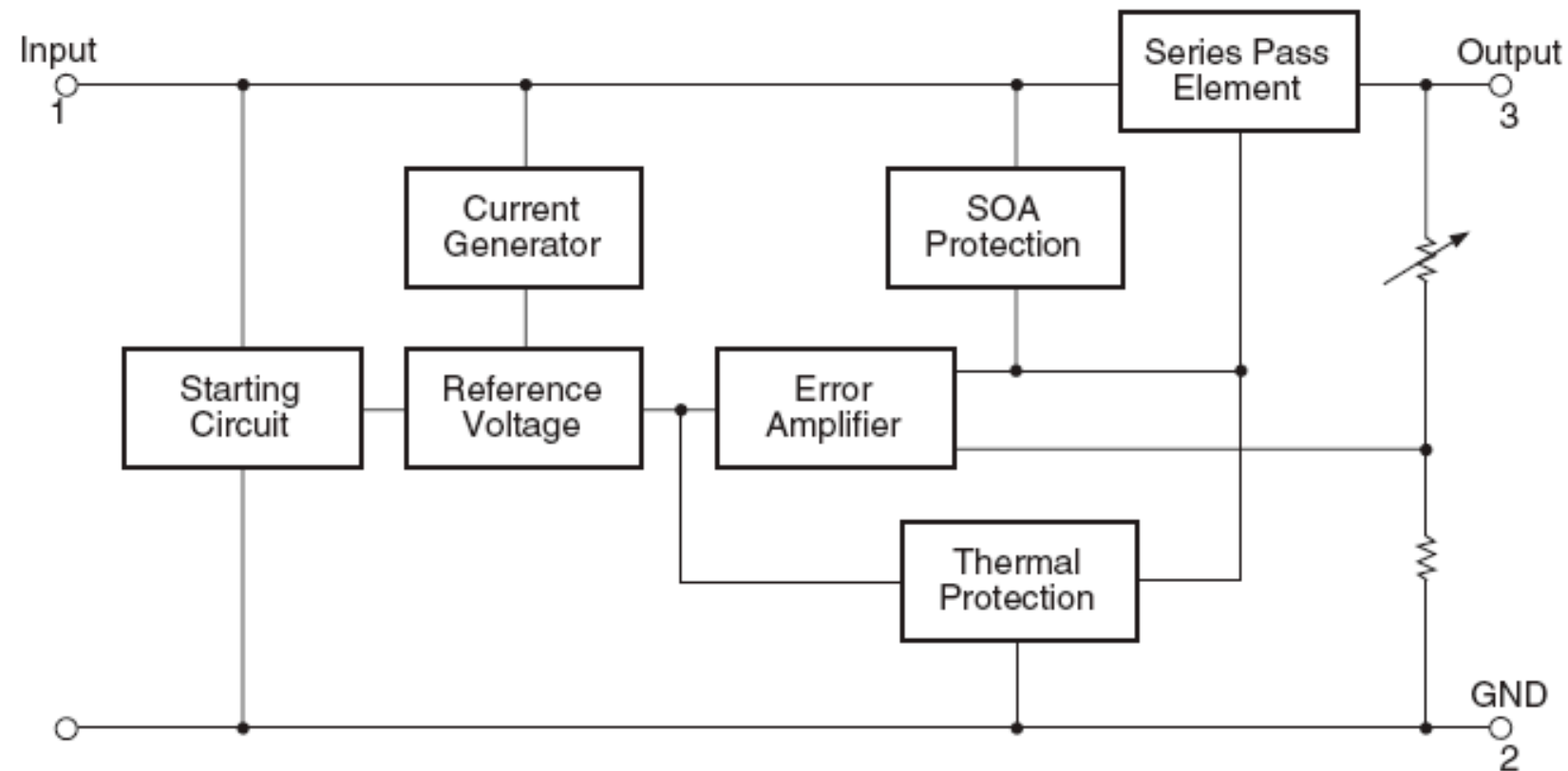


## Fixed Regulator

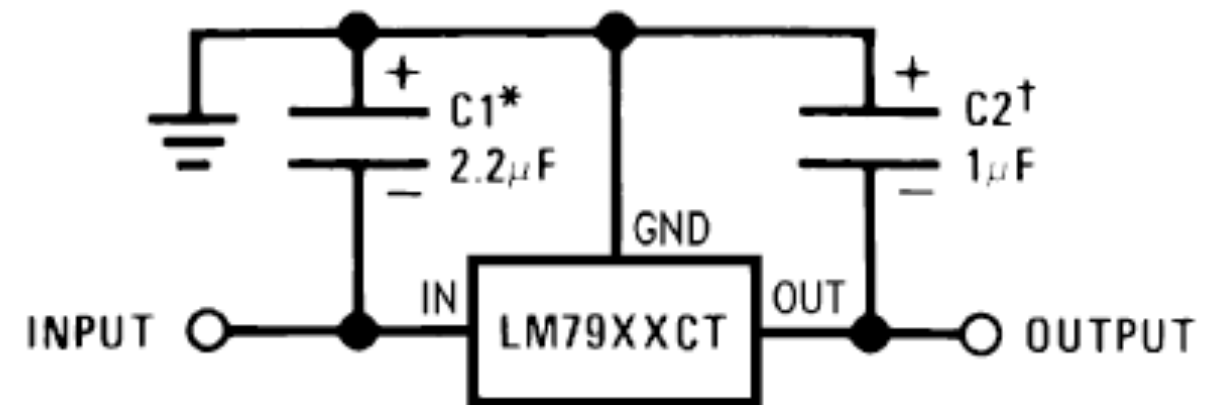


XX=05, 06, 08, 09, 10, 12, 15, 18, 24V

# Adjustable voltage regulators



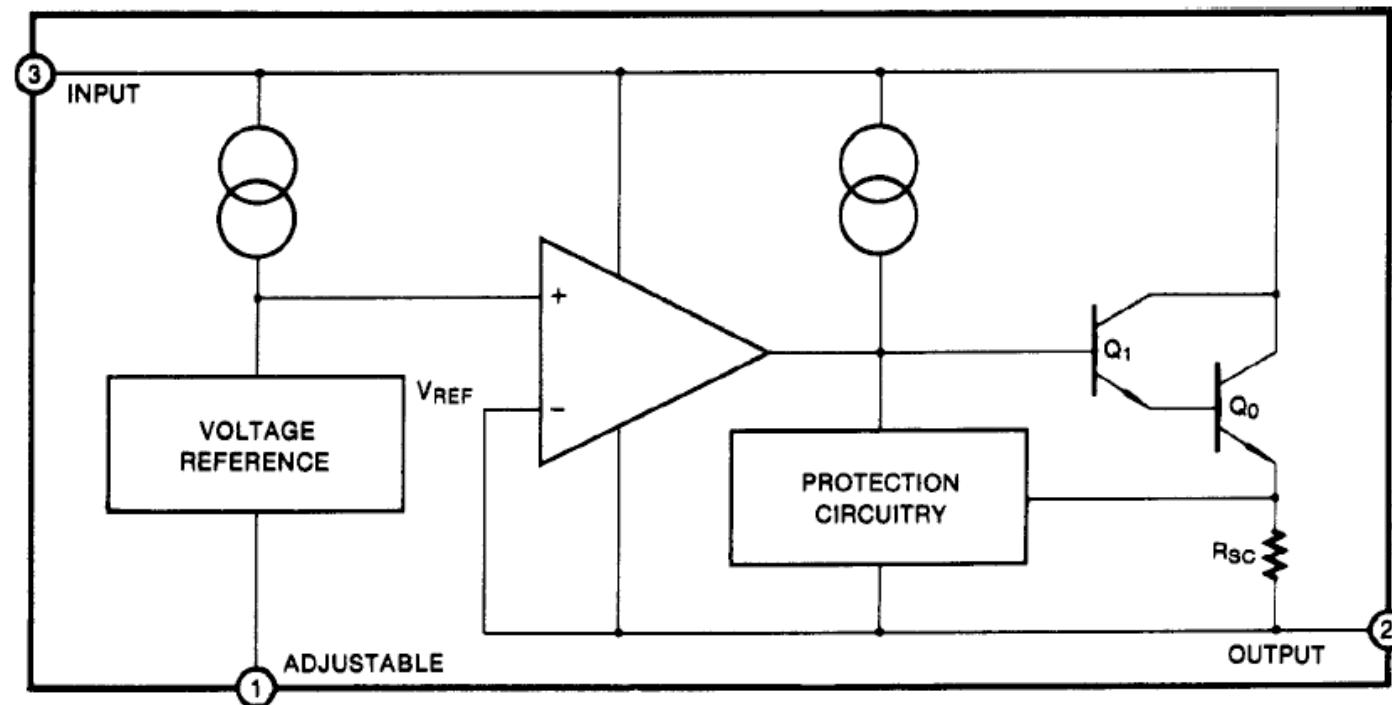


LM350: 3V-35V




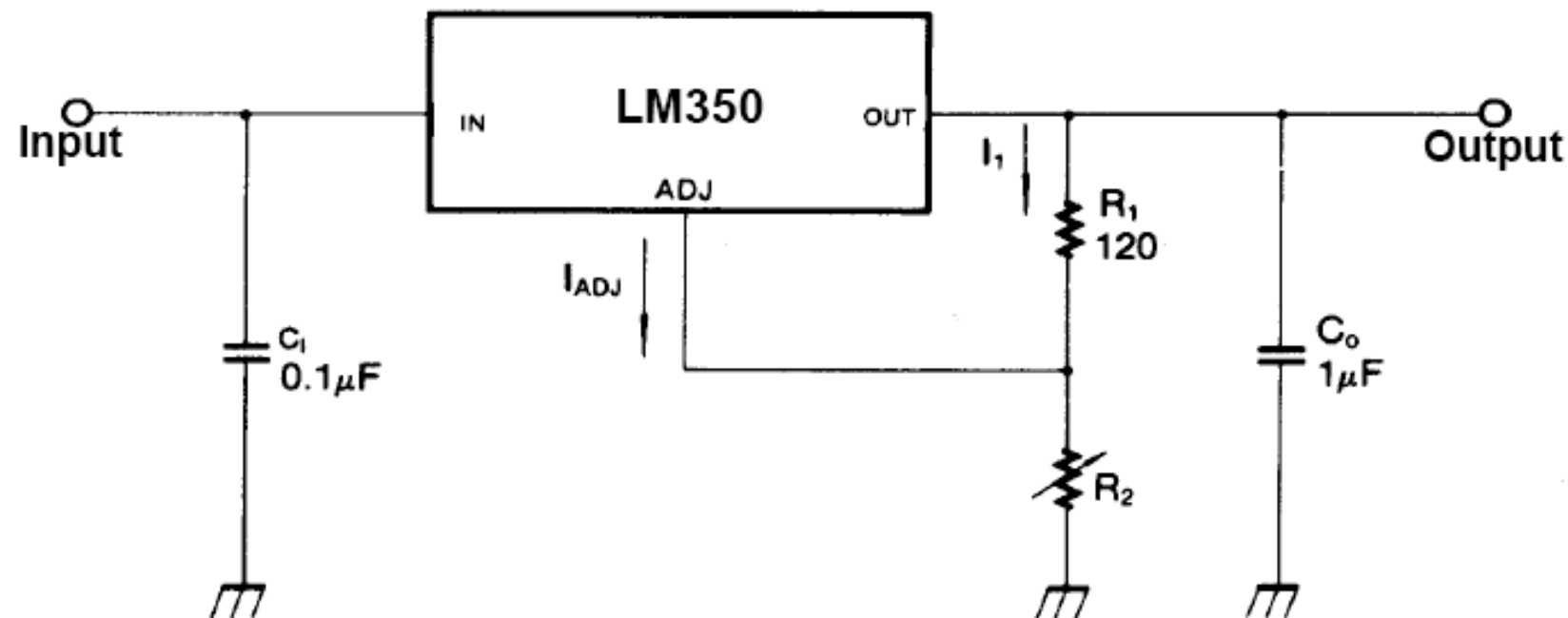







# Current sources

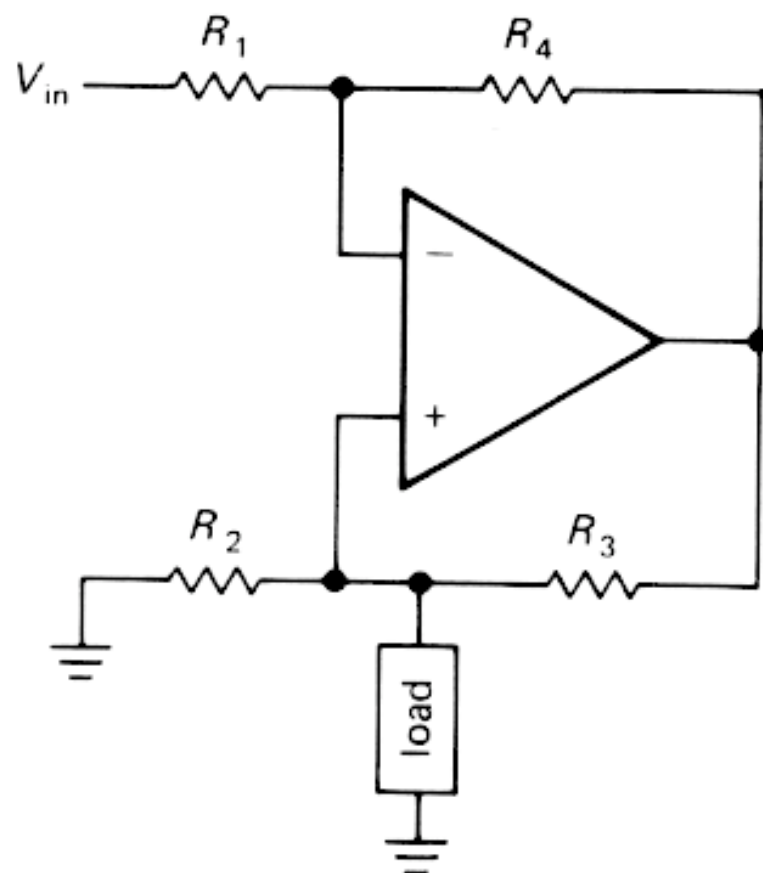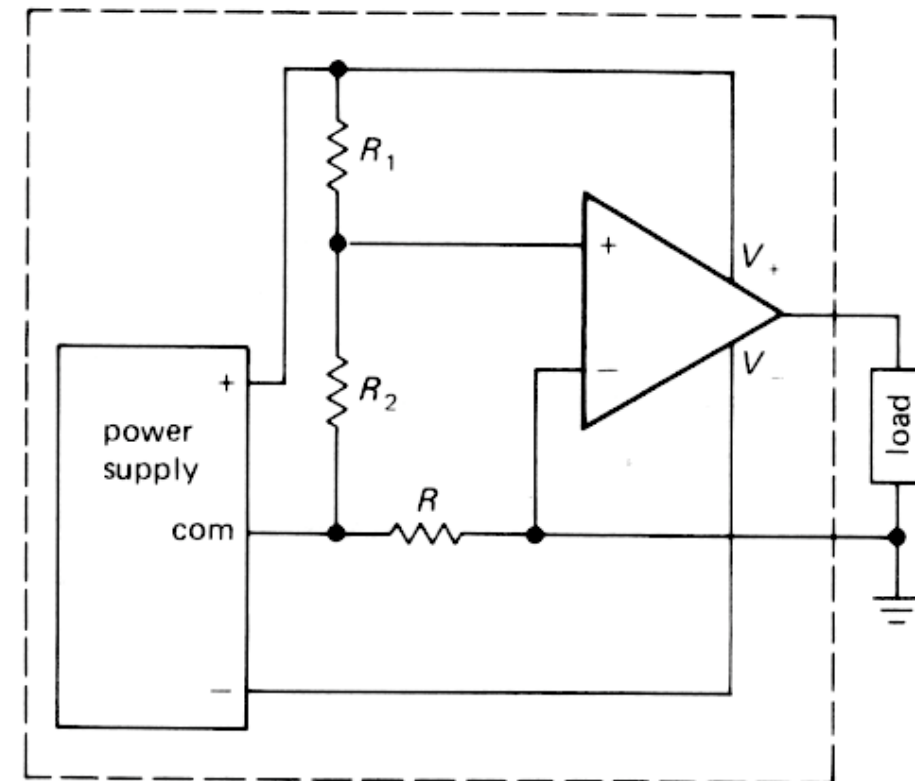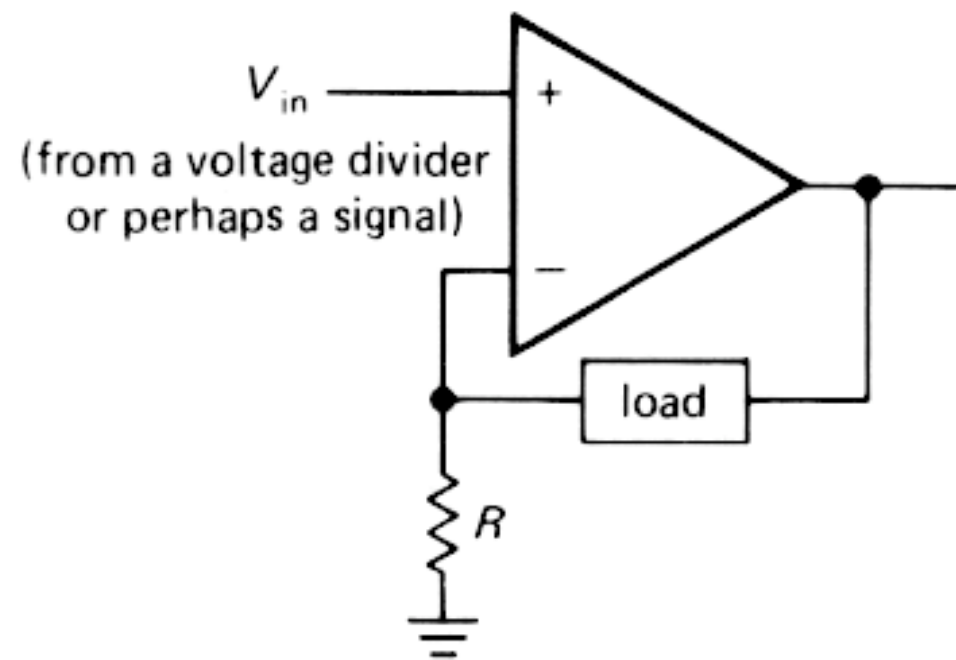


# Electrometers

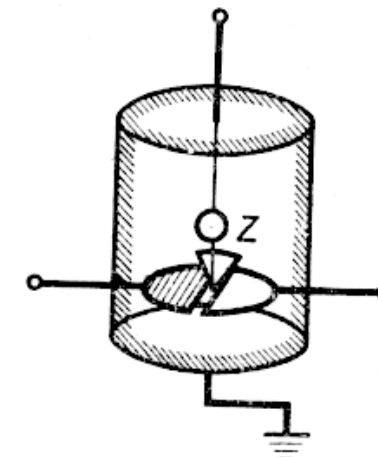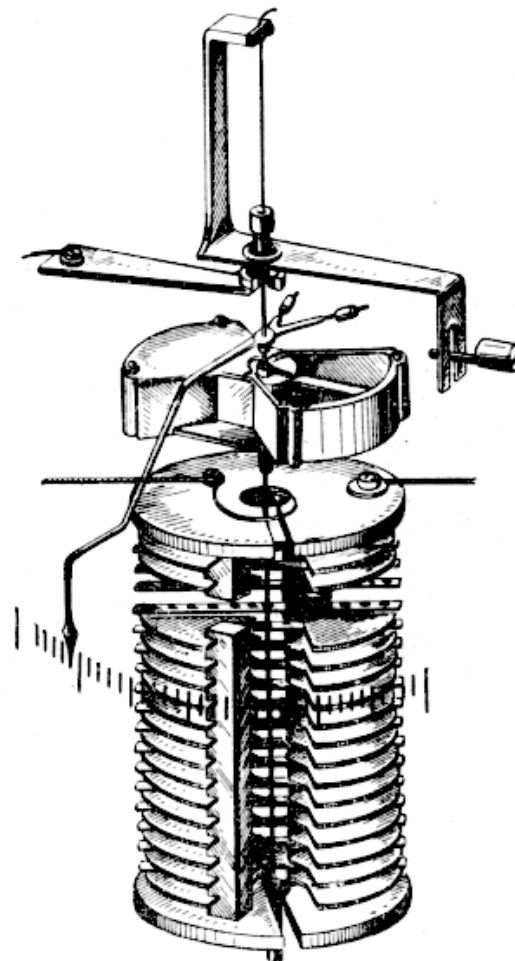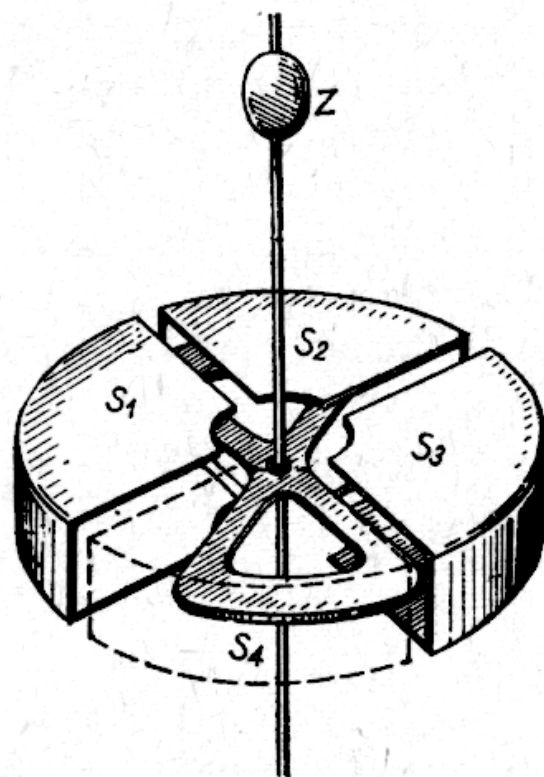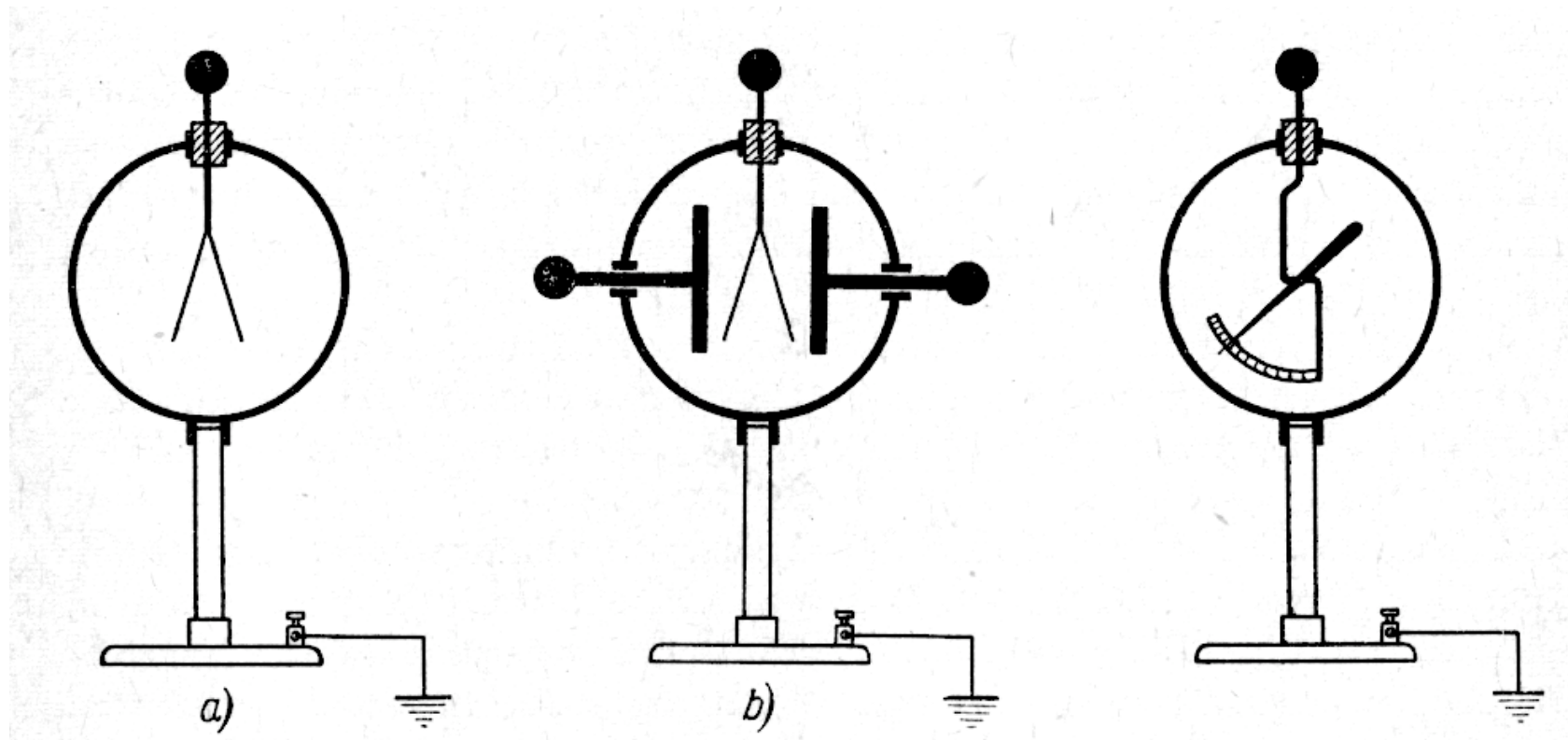

# Current meters

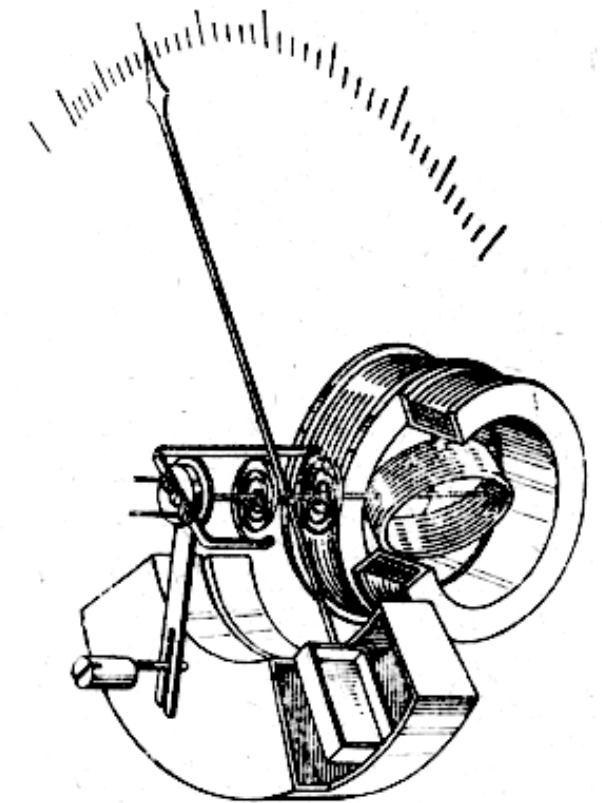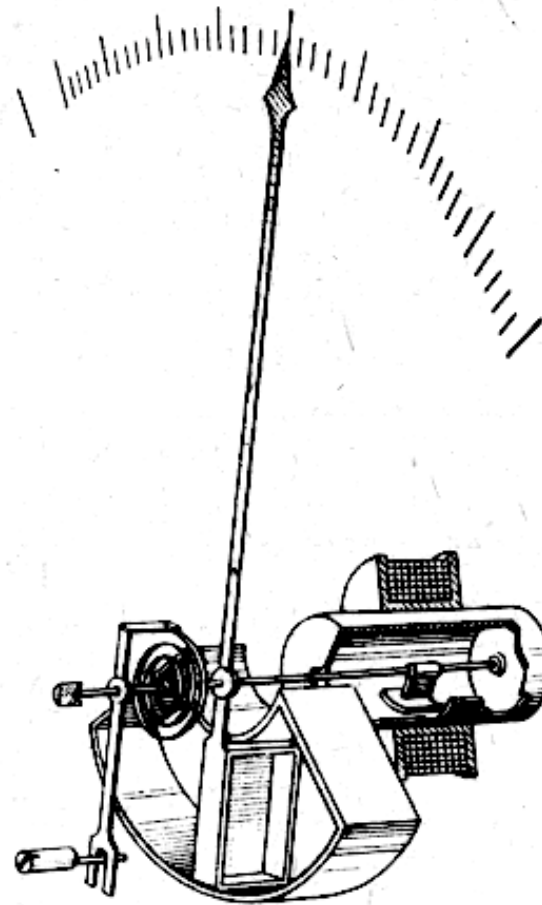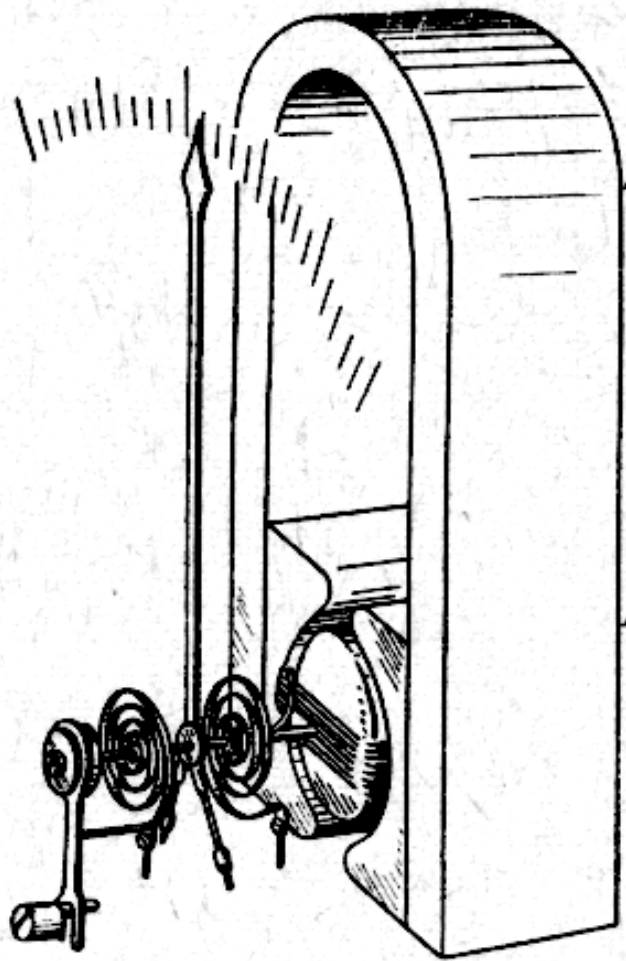


# Digital volt meter (DVM)

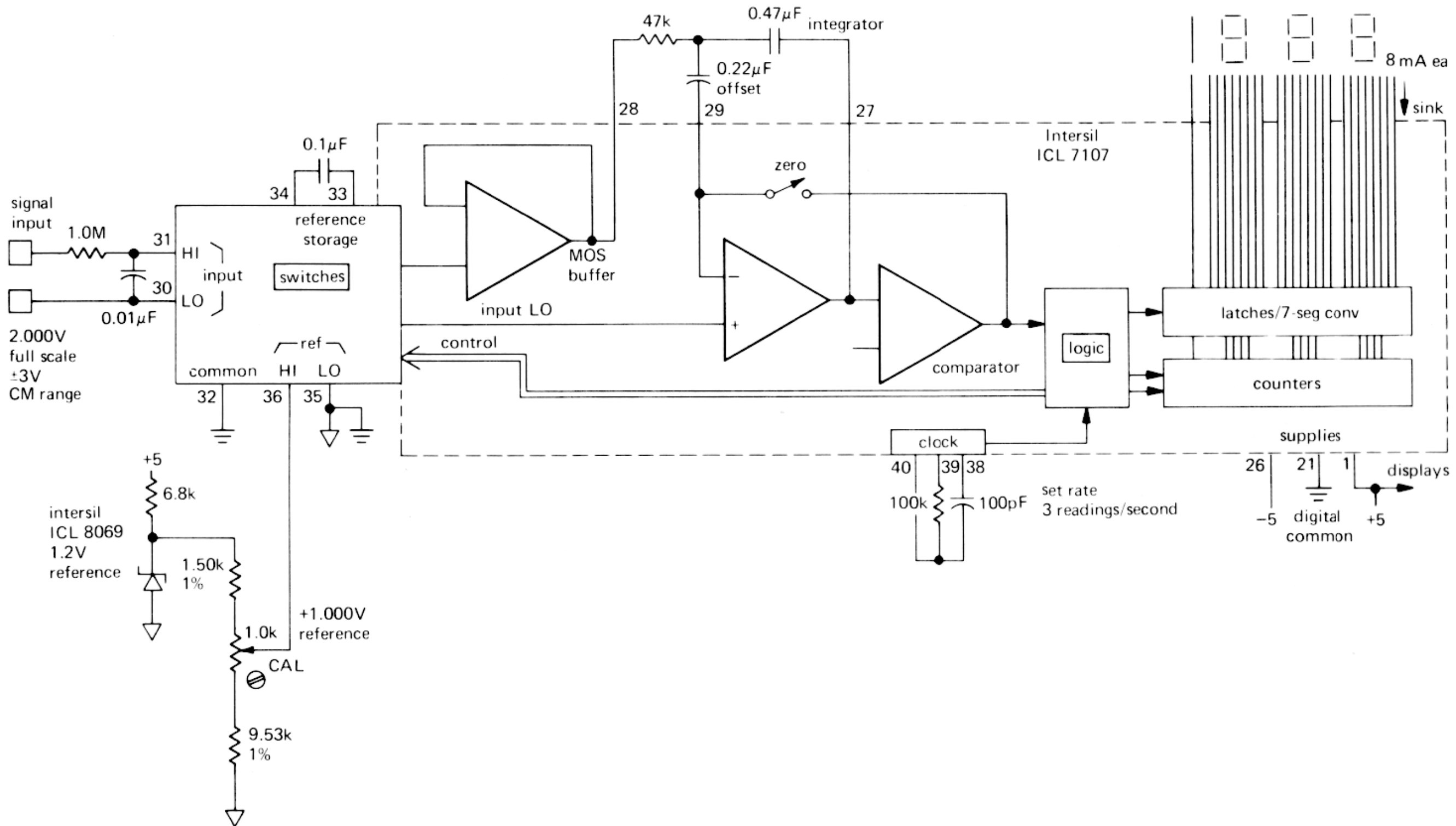





# Digital to analog converters (DAC)

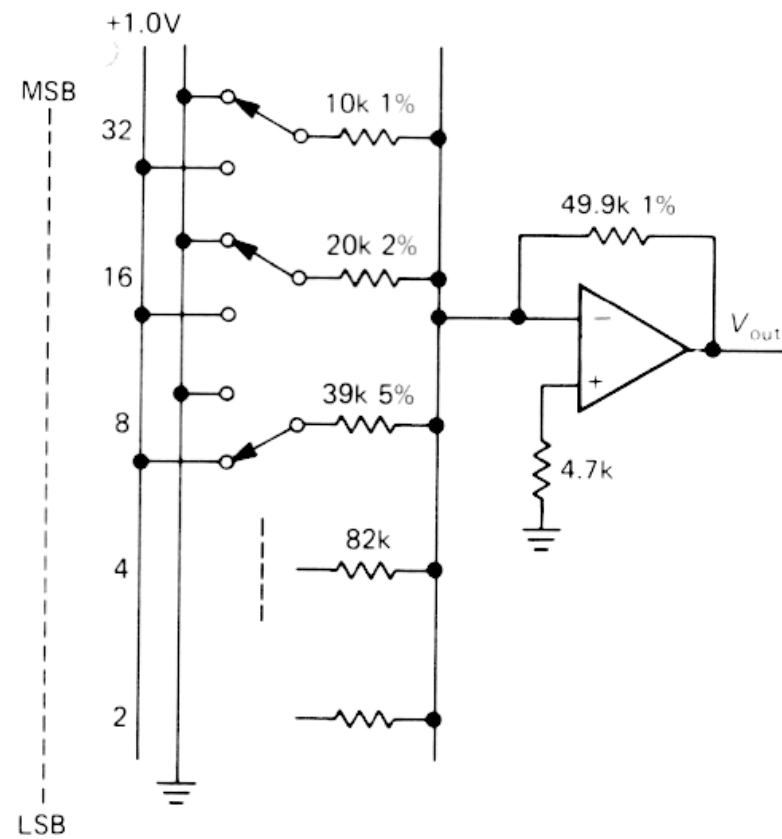


to  
comparator  
input

controls from SAR

256 equal resistors

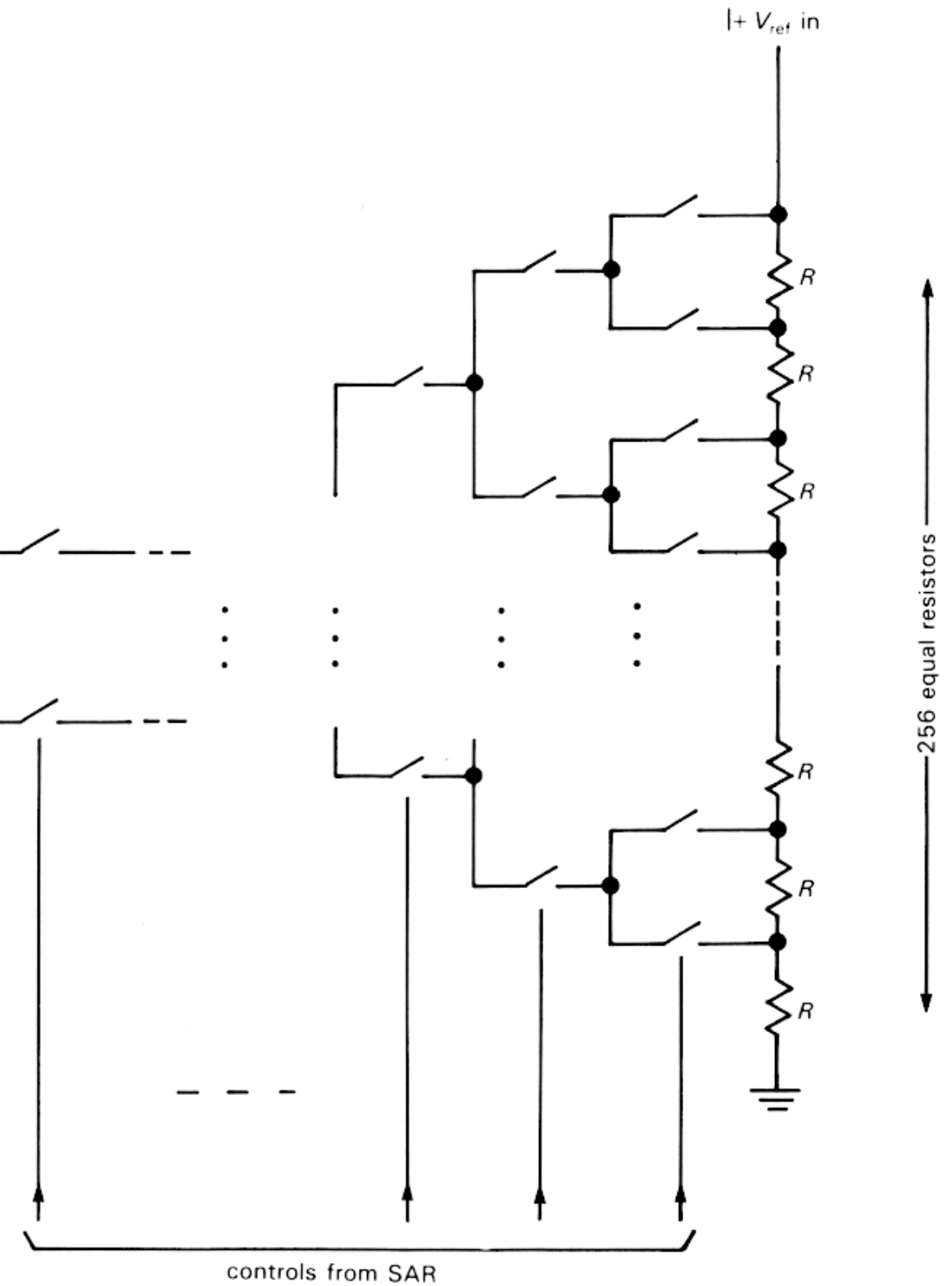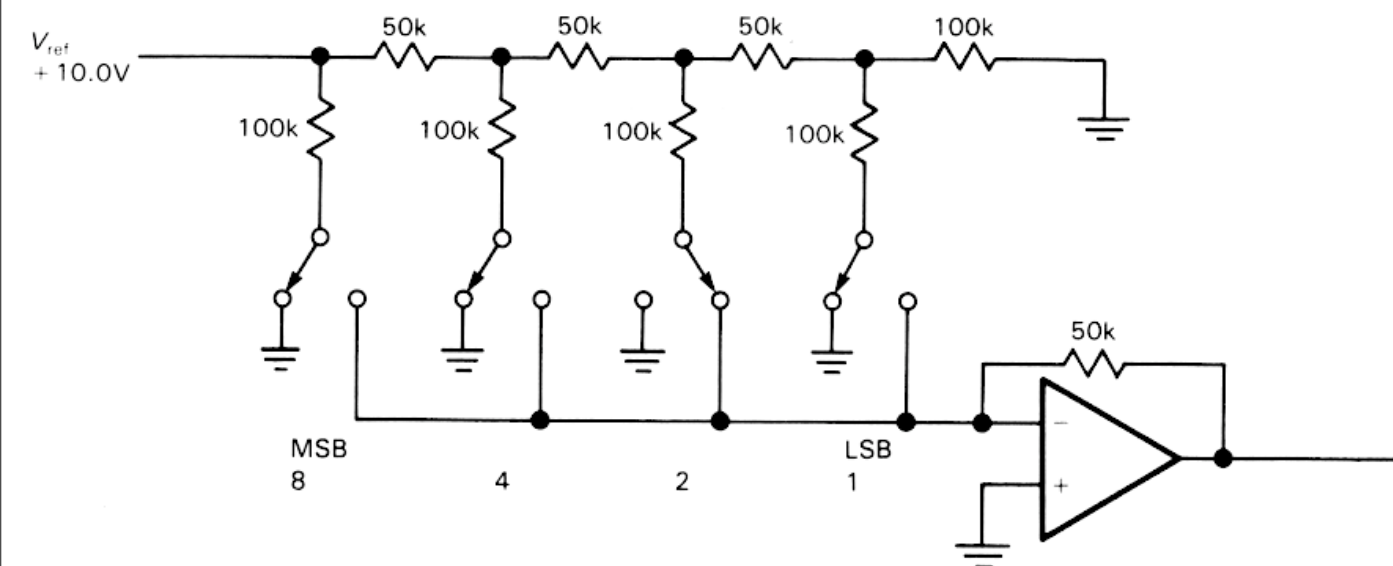

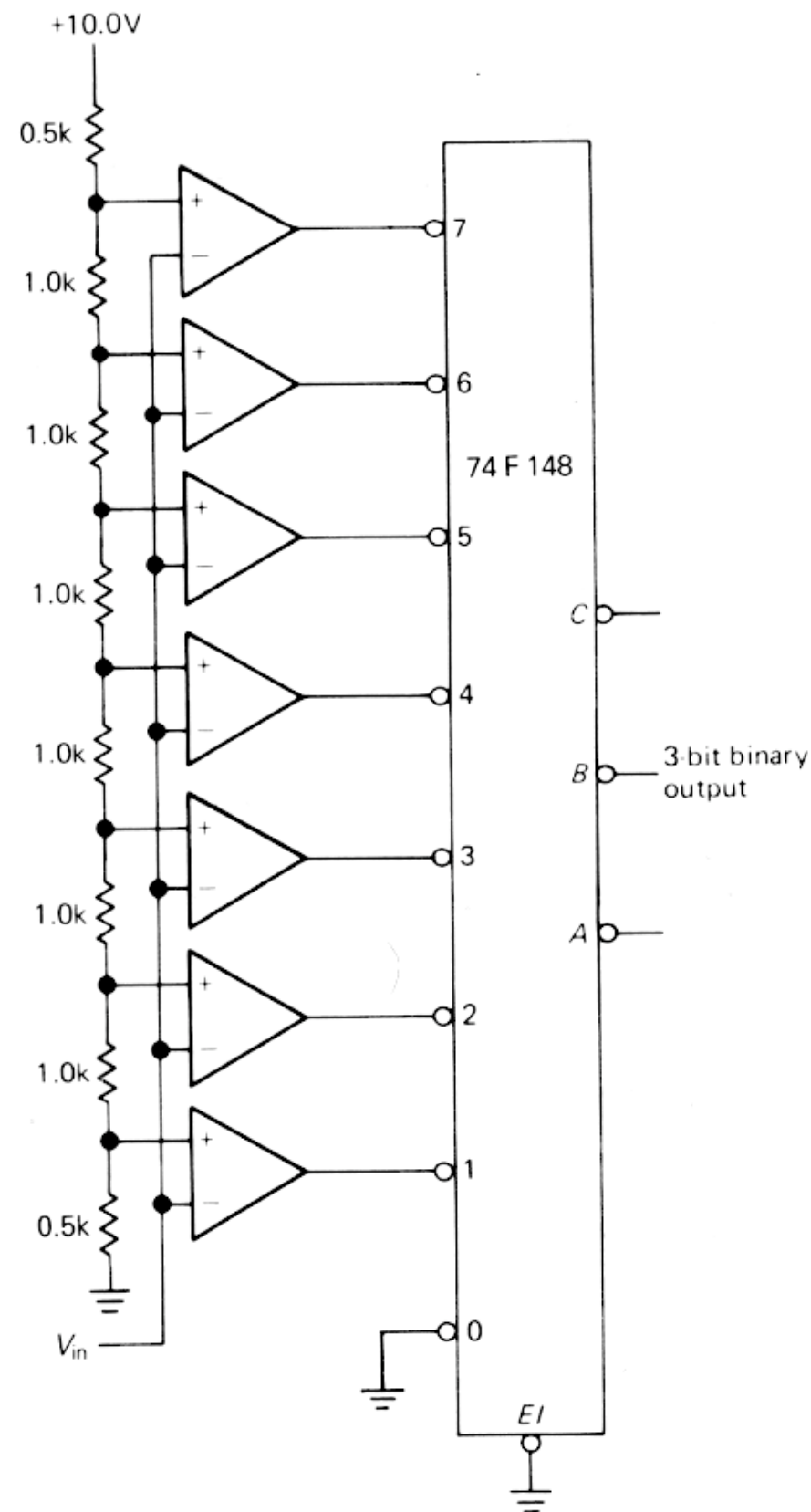
# Analog to digital converters (ADC) - flash




# Analog to digital converters (ADC)

## "voltage to time"

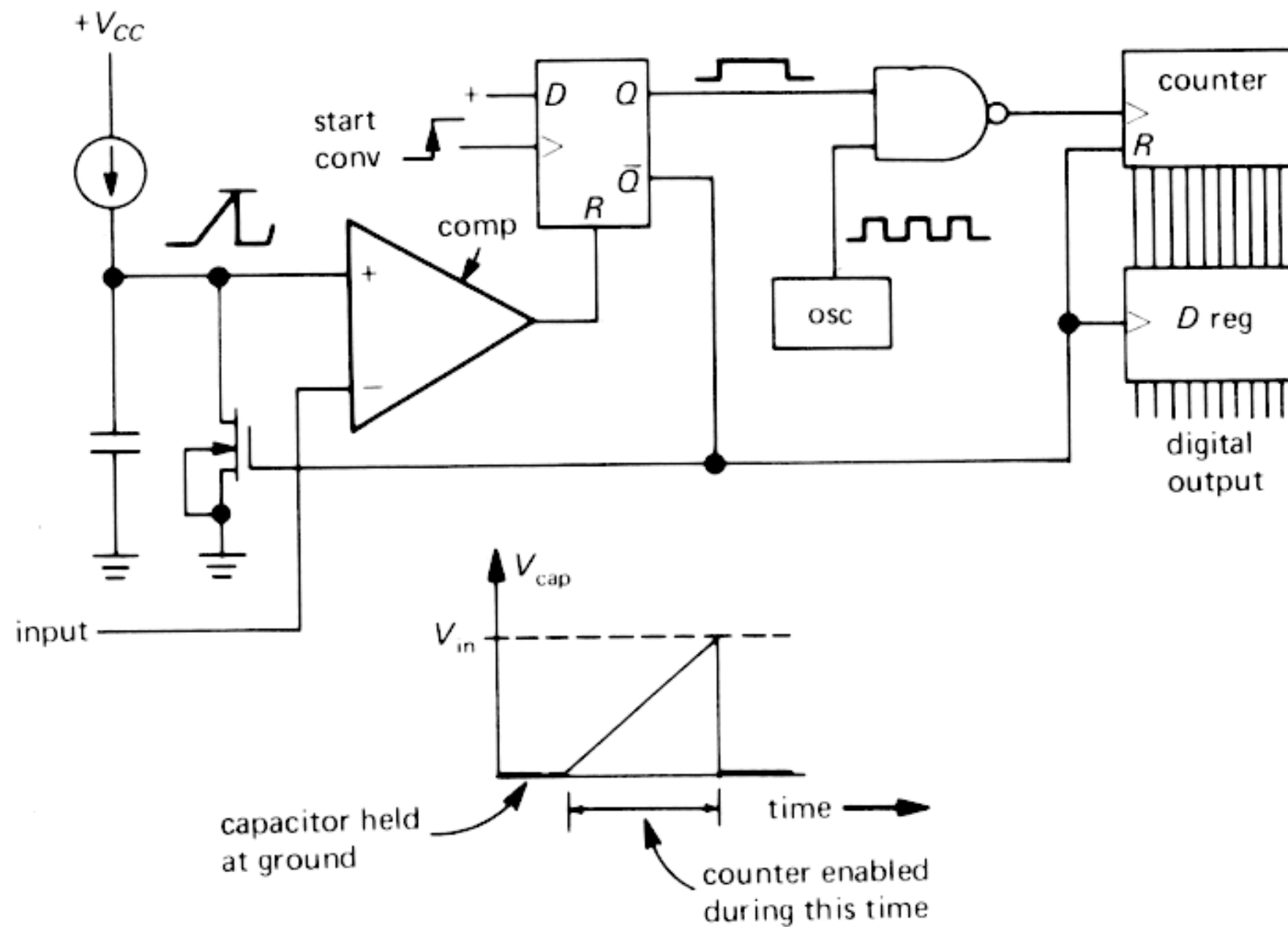


# Analog to digital converters (ADC)

## "successive approximation"

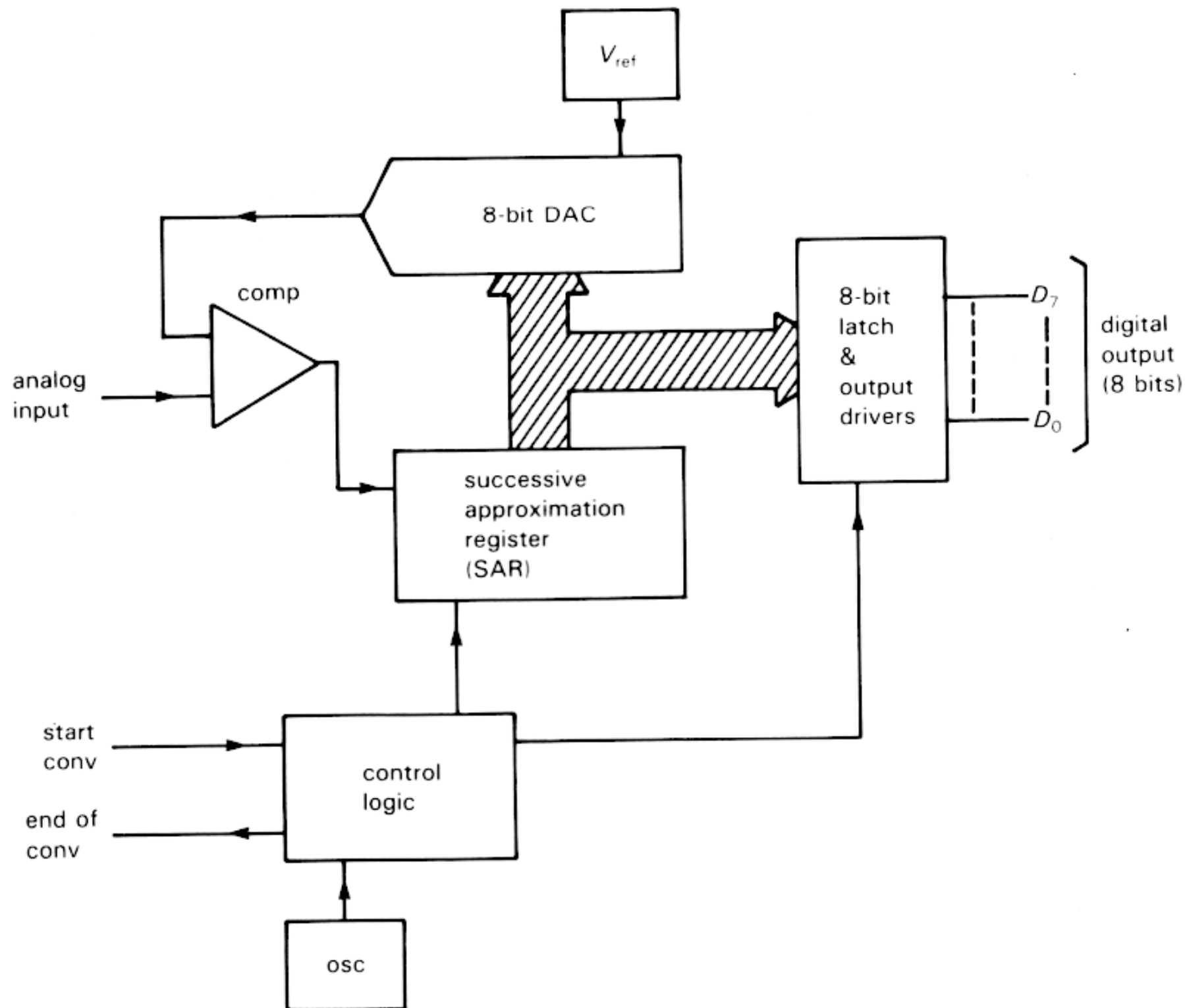




# "Sample and hold circuit"



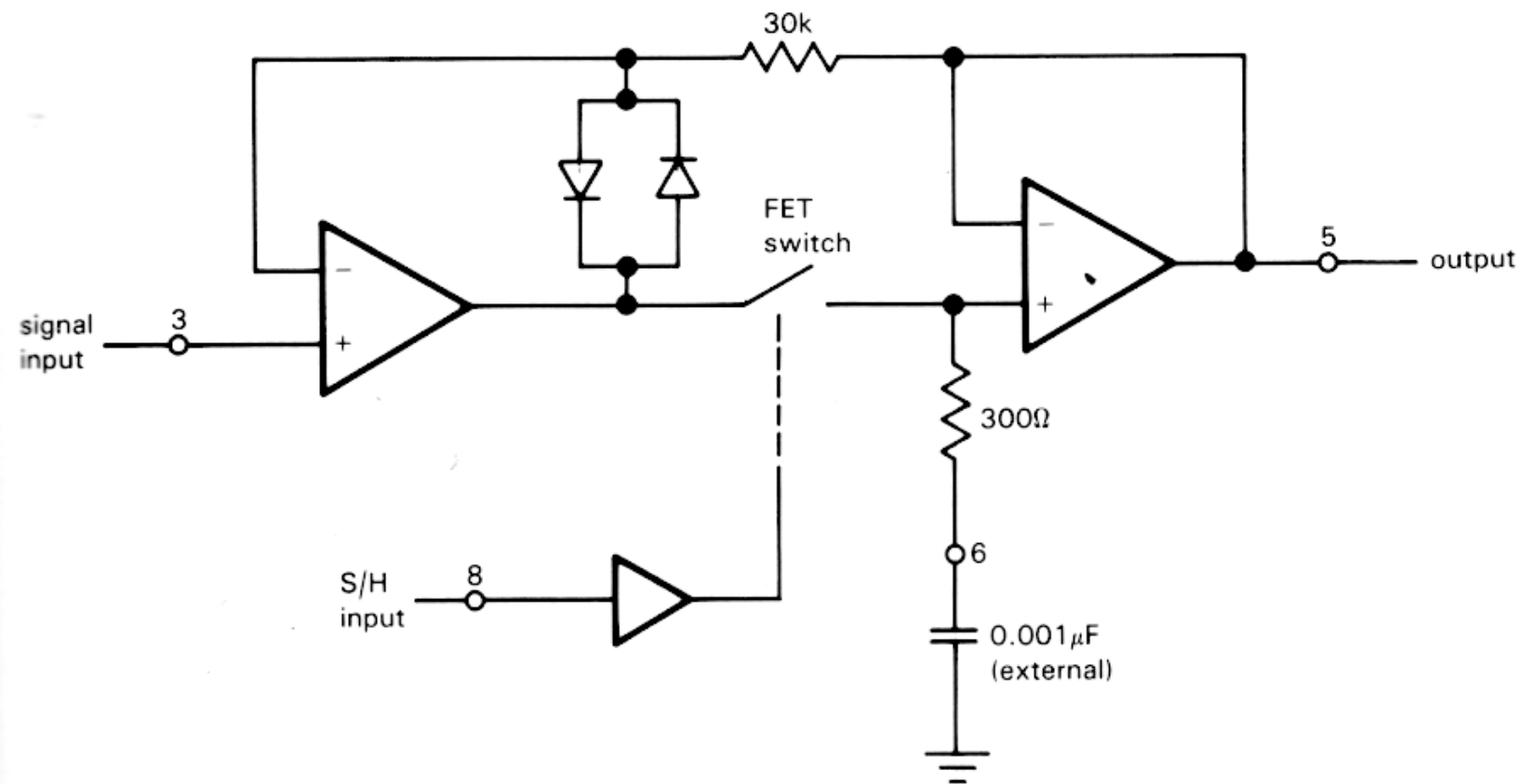


B

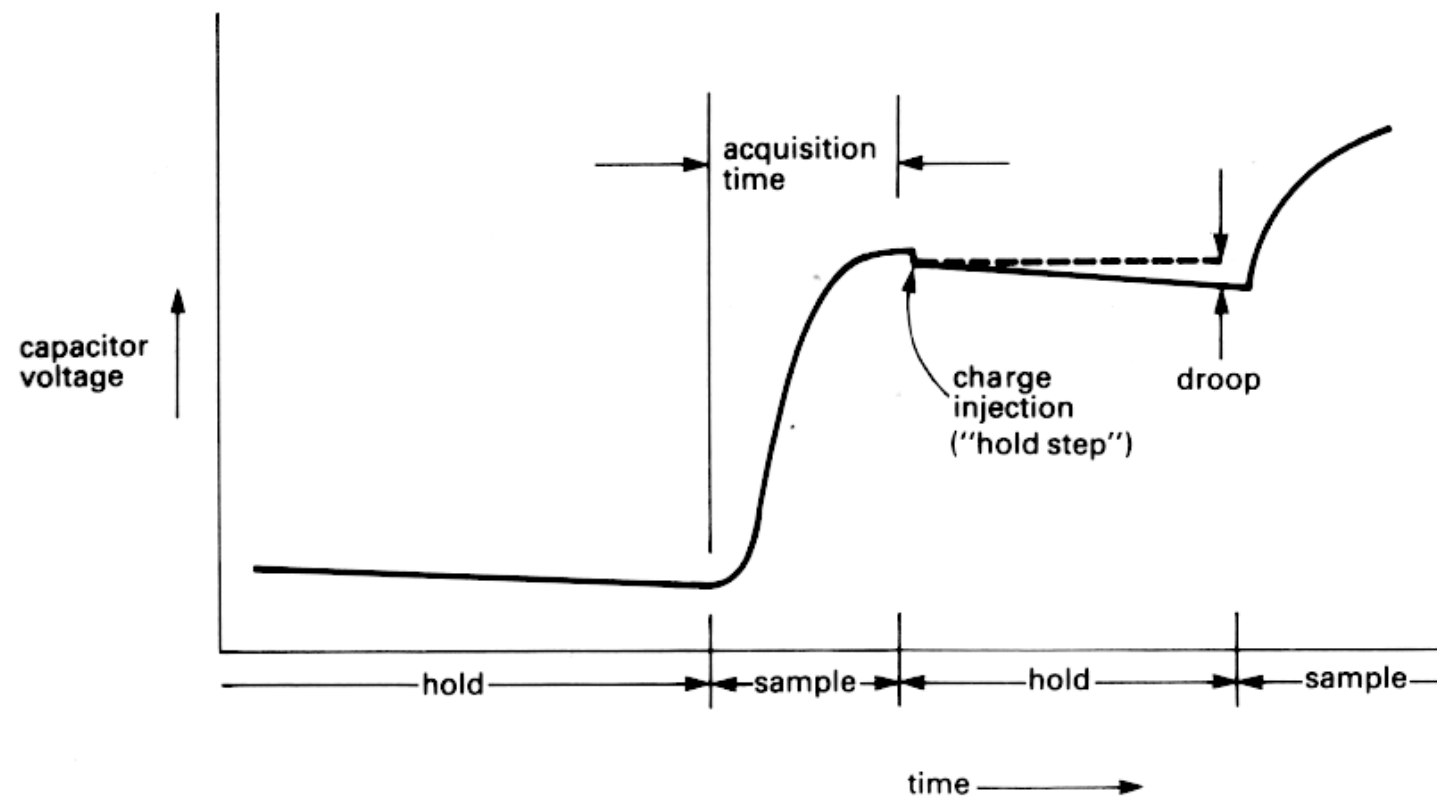


A


# Signal amplification (OpAmps)

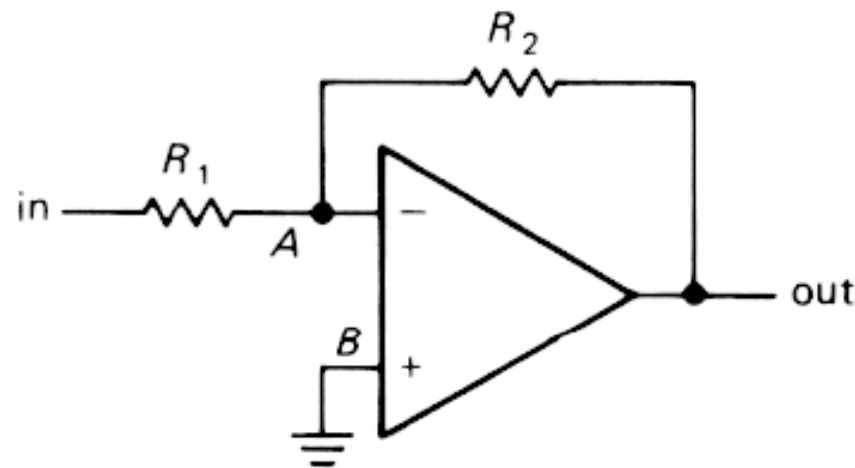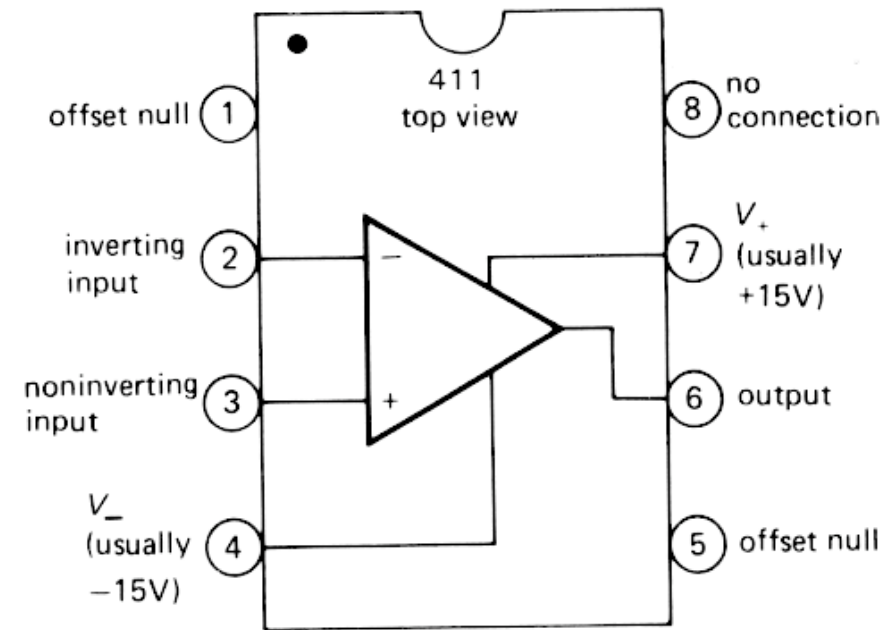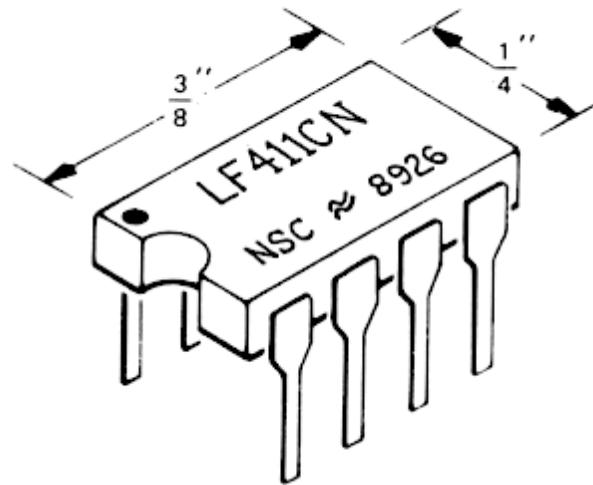

Inverting amplifier

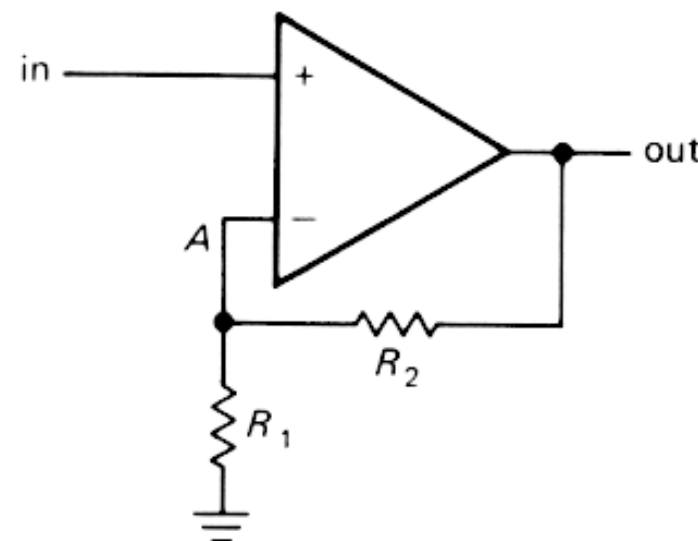


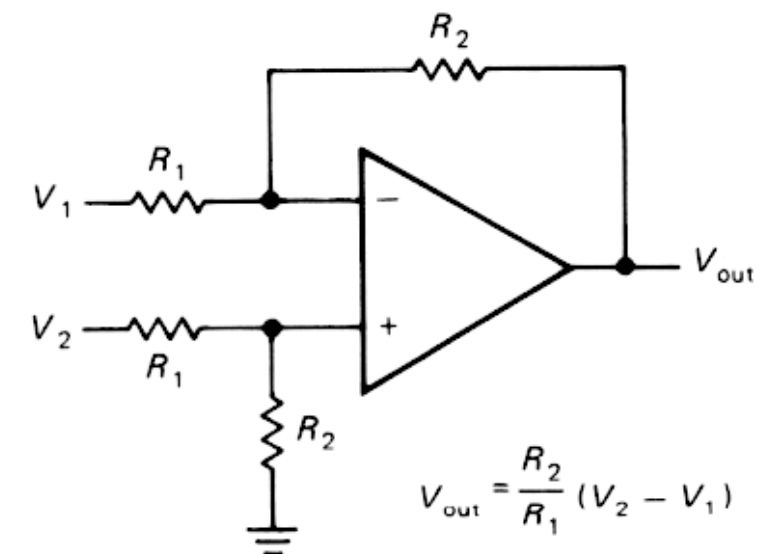Non-inverting amplifier  
- "voltage follower"




Differential amplifier


# LF411 internal schematics

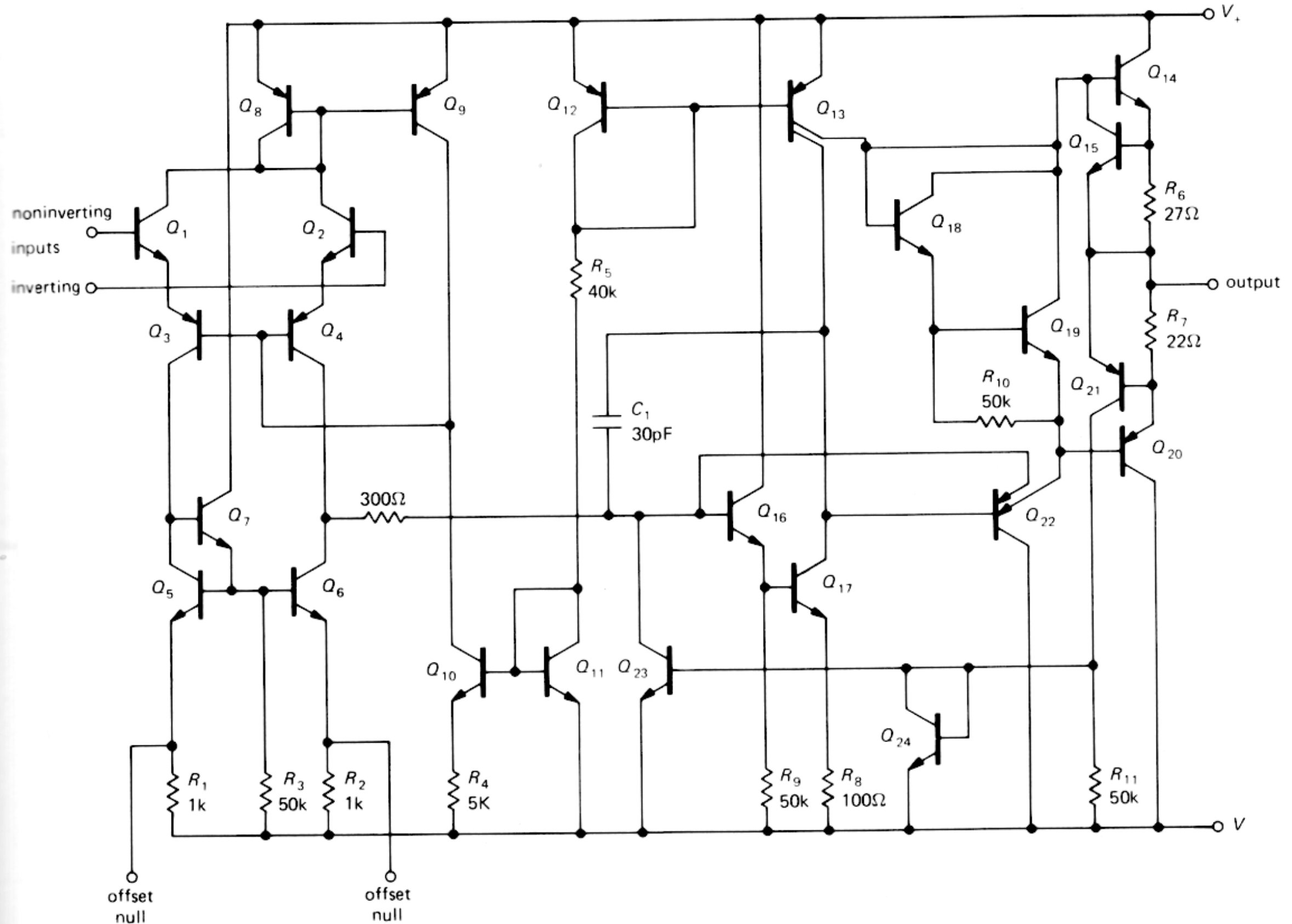

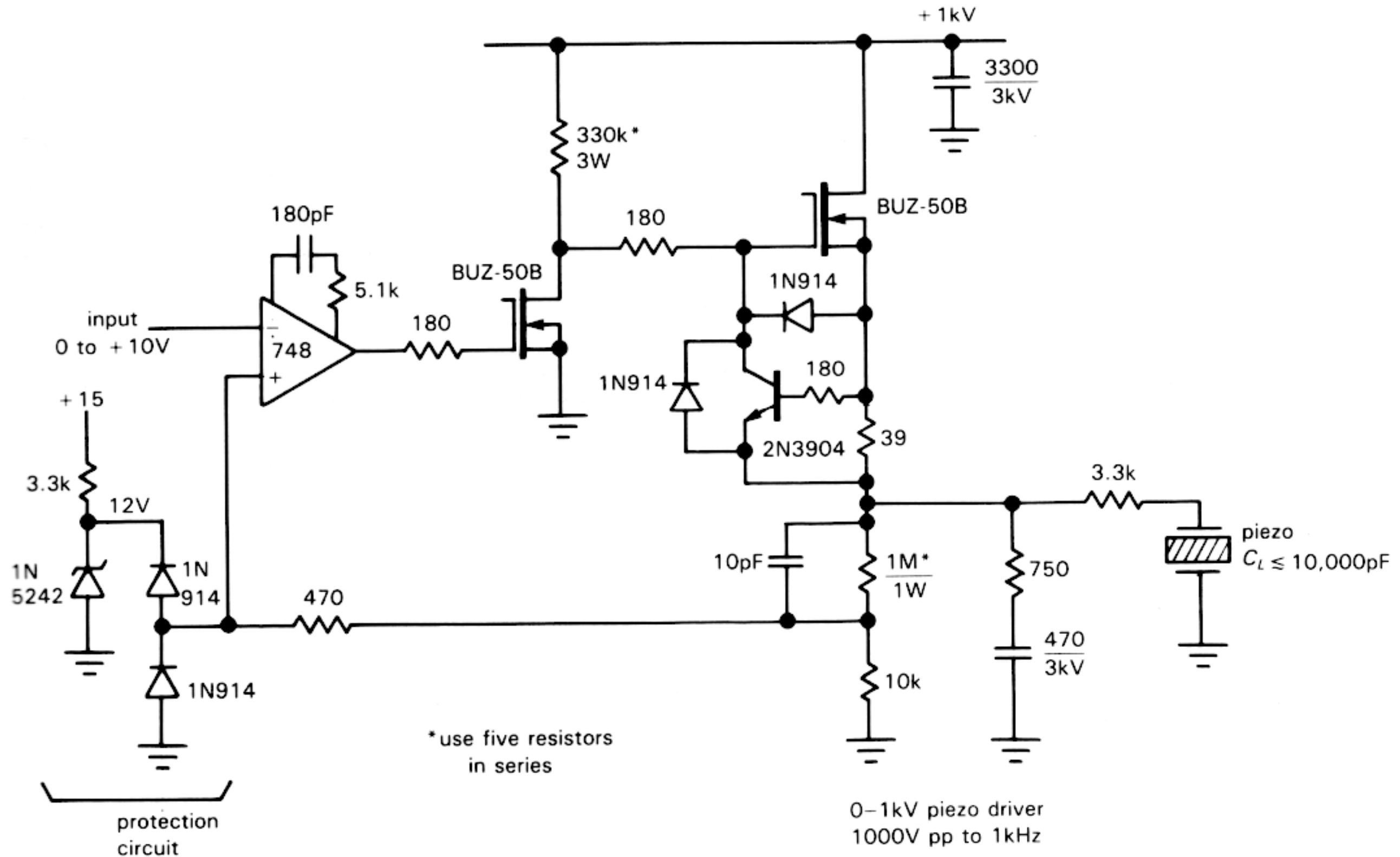
# Example - 1kV piezo driver ( $2V/\mu s$ )



# Oscillators

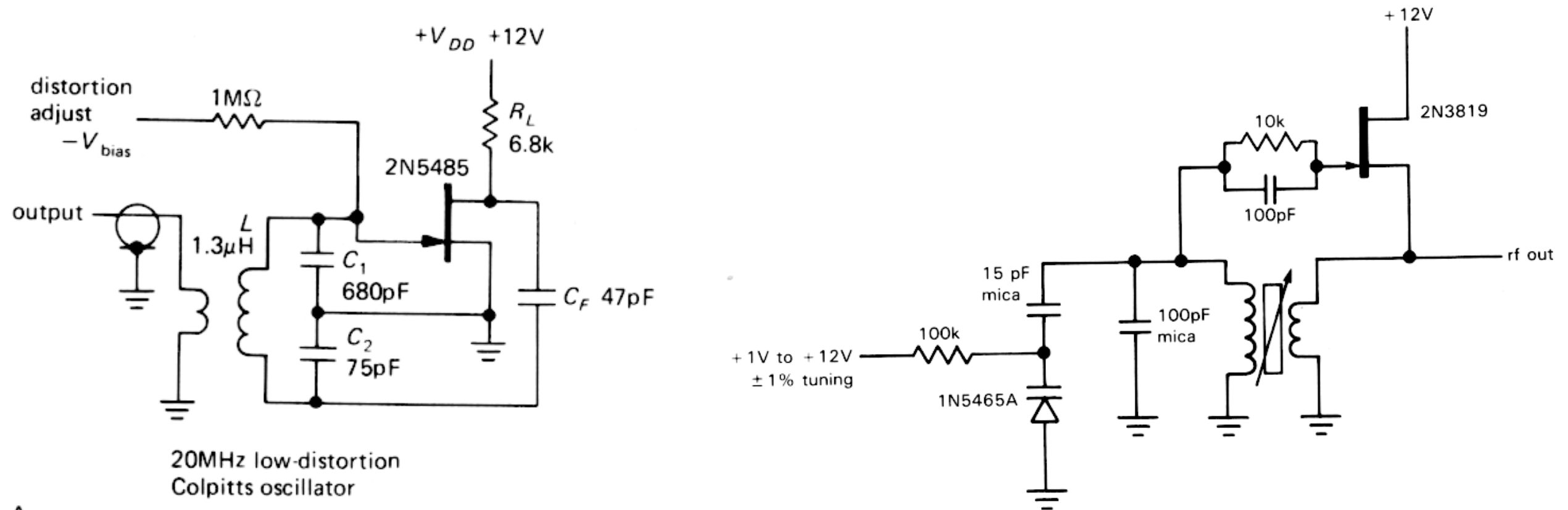

A


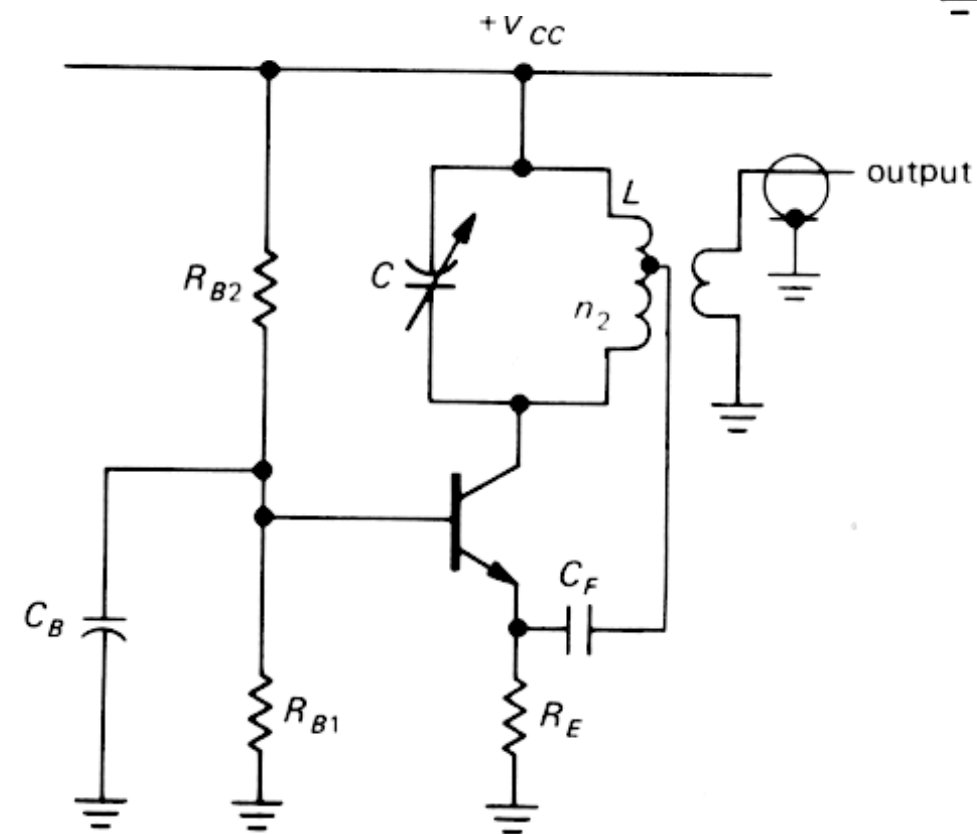


B


Hartley LC oscillator

C


# Single chip oscillator

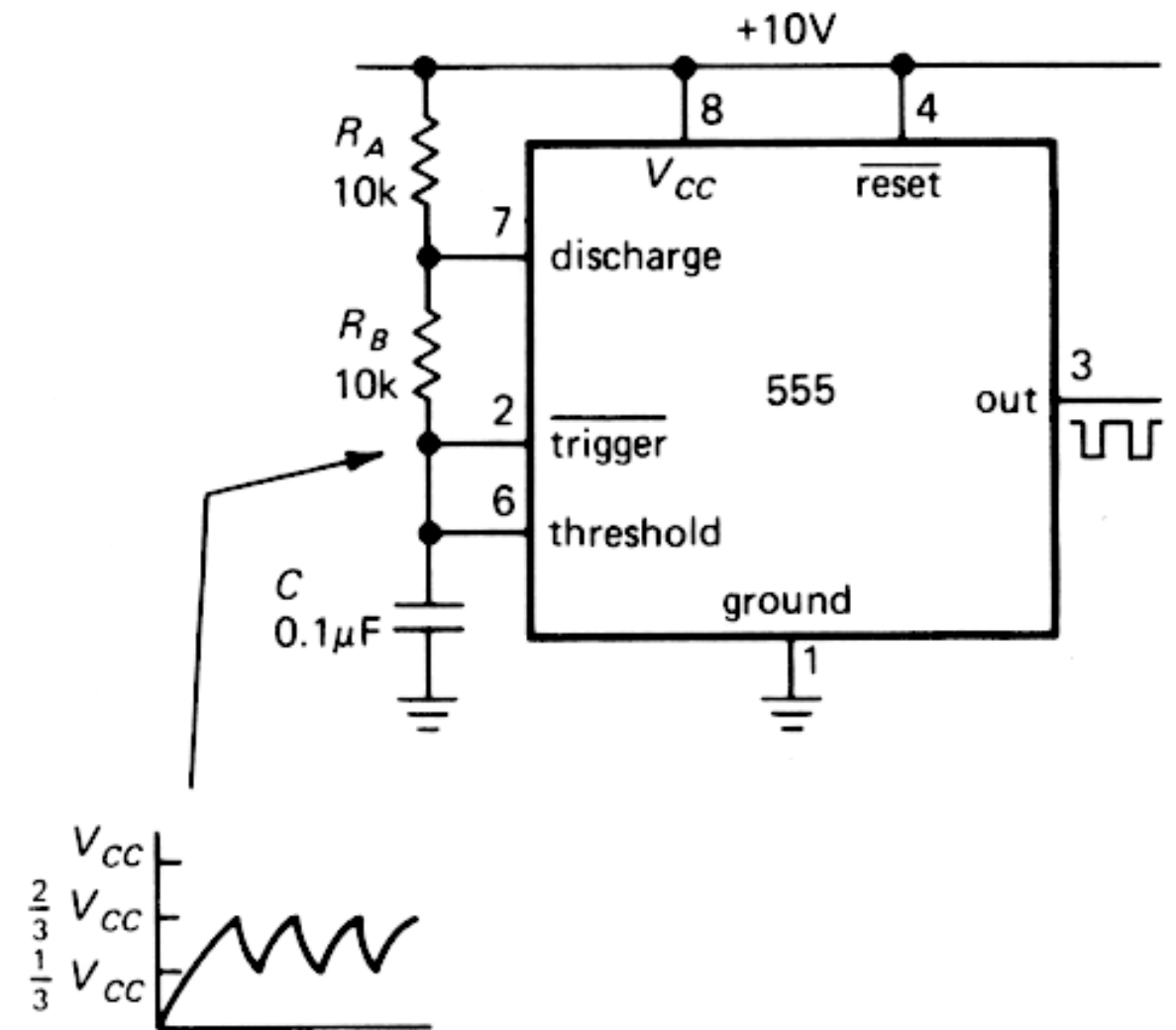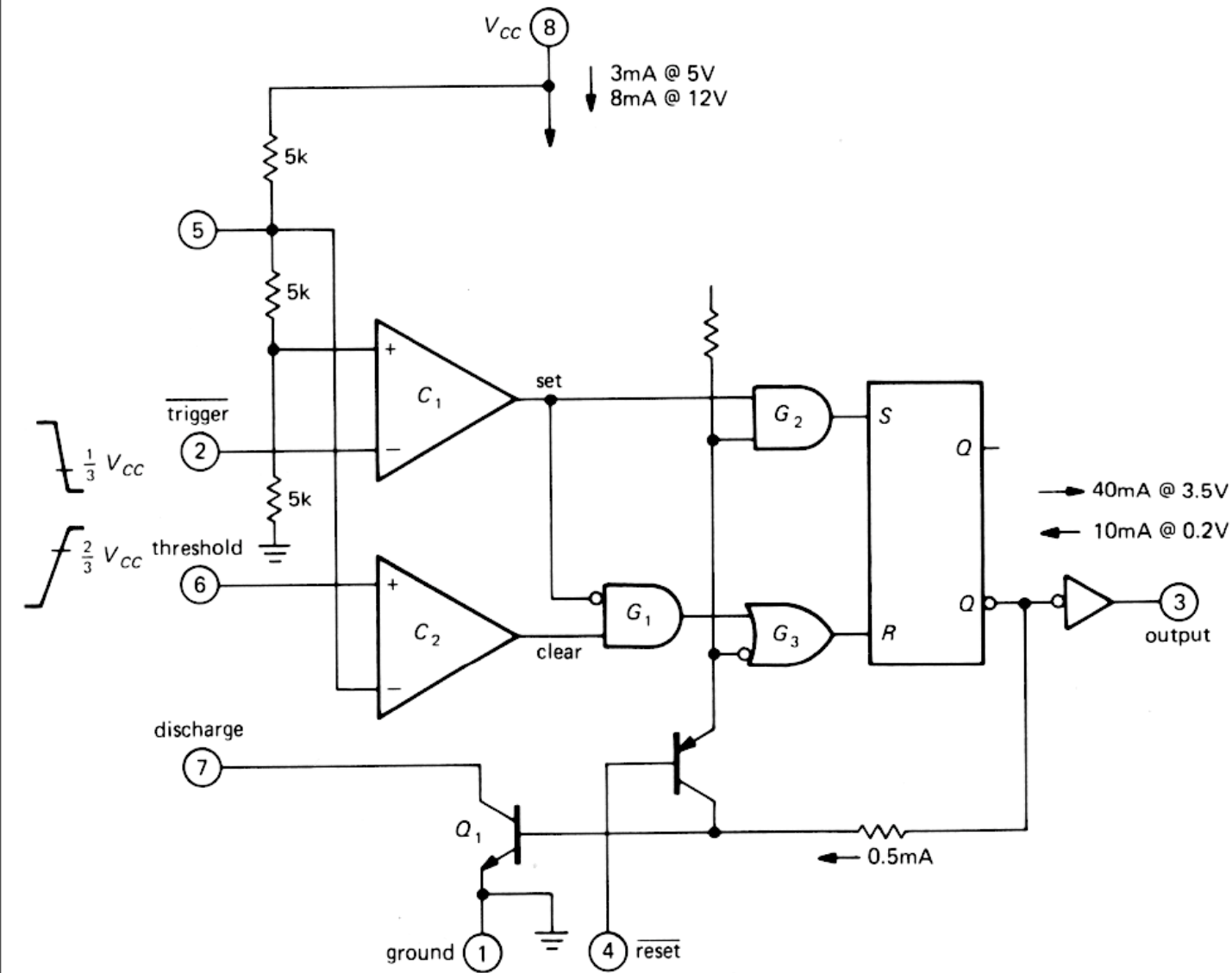


# Quartz oscillators

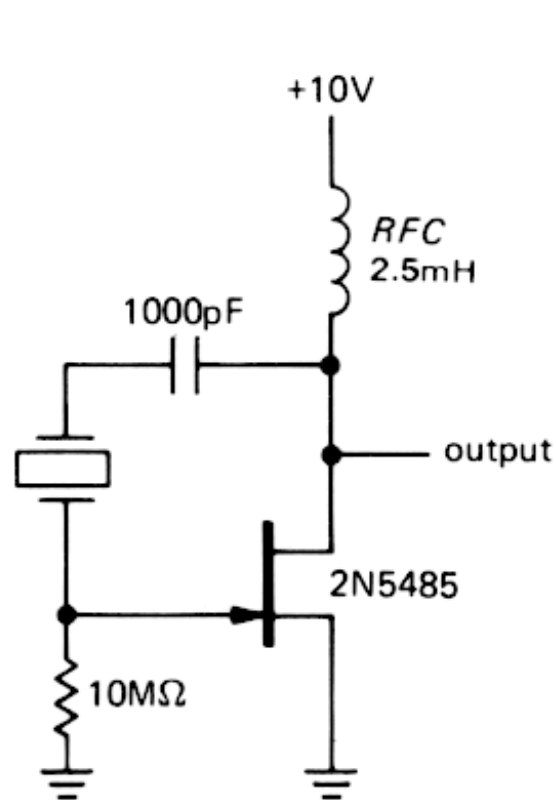


A. Pierce oscillator

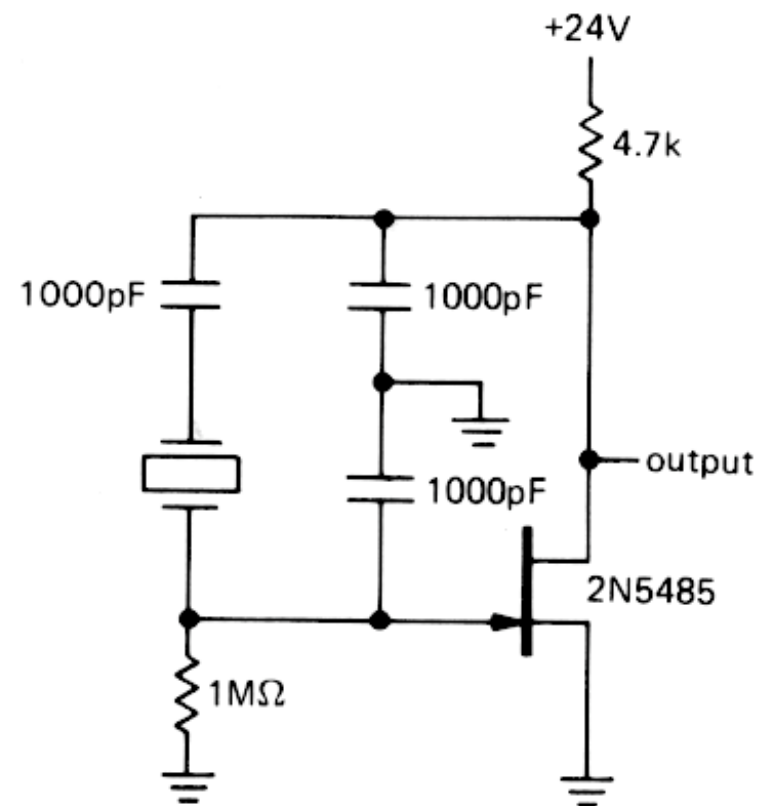


B. Colpitts oscillator

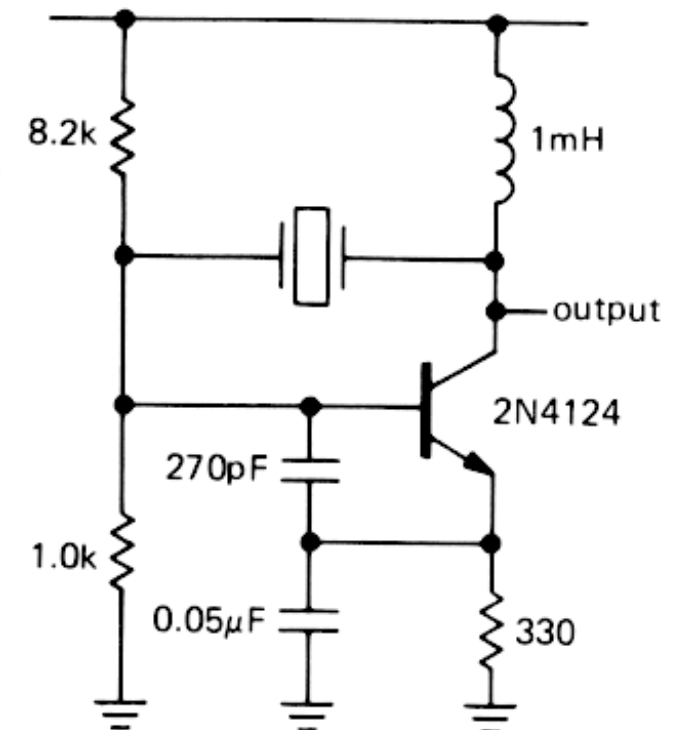

C

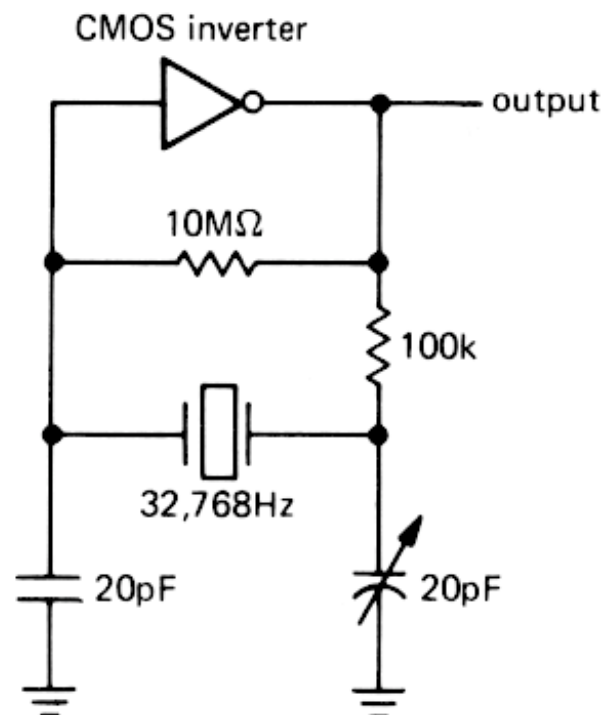

D

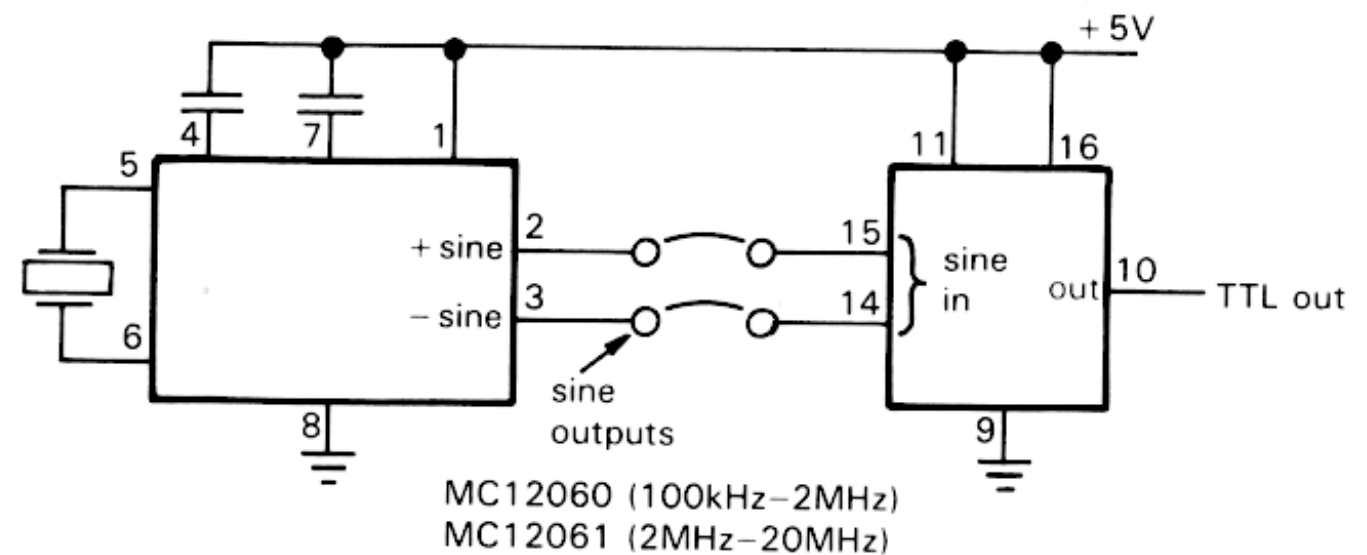

E

# Noise reduction techniques

## Main sources of noise:

1) interference excitation of currents in circuit due to EM waves

2) Johnson noise - thermal excitation in resistors:

$$V_J = (4kTRB)^{1/2}$$

e. g.  $T=300$ ,  $R=10k\Omega$ :  $V_J=1.3 \mu V$



3) shot noise (due to quantization of charge)

$$I = (2eI_{dc}B)^{1/2}$$

e. g. at 10 kHz bandwidth

1A current has noise of 57 nA (0.000006%)

1  $\mu$ A current has noise of 6 nA (0.006%)

1pA current has noise of 56 fA (5.6%)

## 4) flicker noise $1/f$

### Resistors

Carbon composite

$0.1 \mu V - 3.0 \mu V$

Carbon film

$0.05 \mu V - 0.3 \mu V$


Metal film

$0.02 \mu V - 0.2 \mu V$


Wire wound

$0.01 \mu V - 0.2 \mu V$

# Grounding


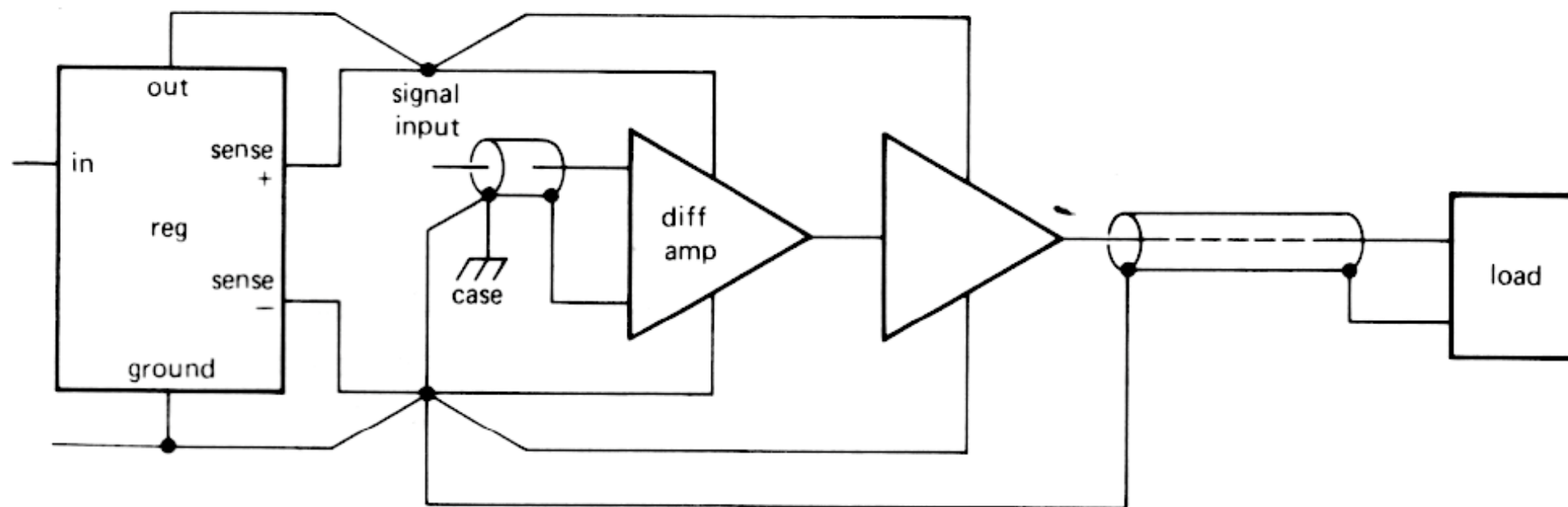


A


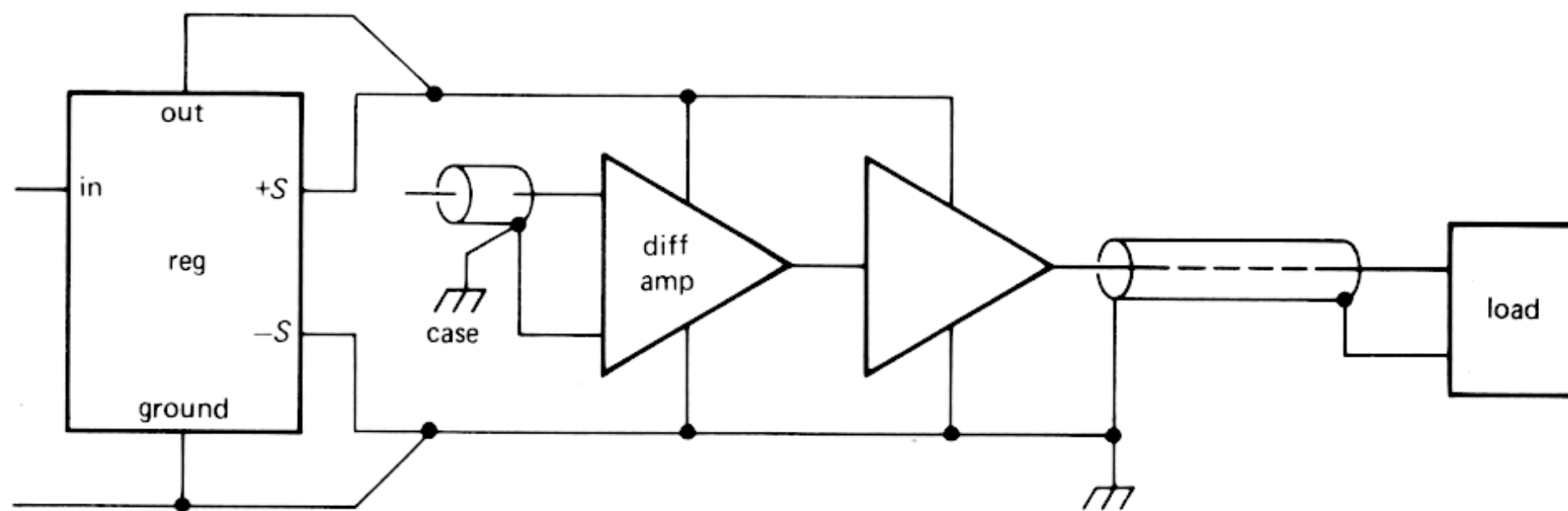


B


# Grounding

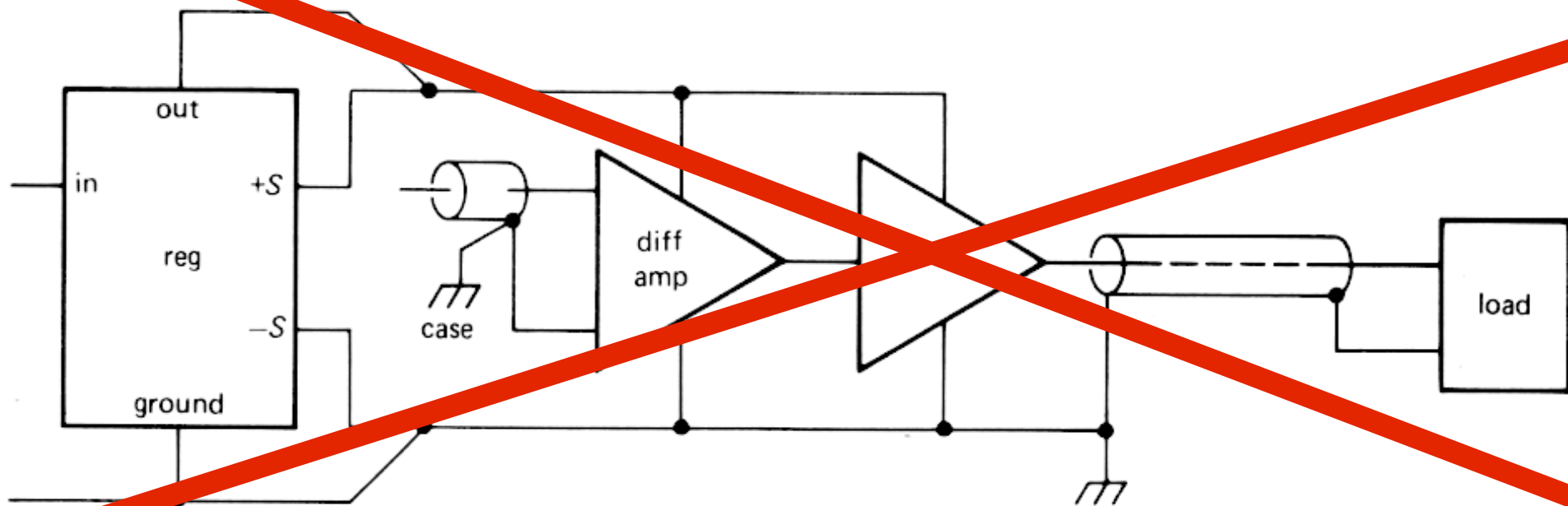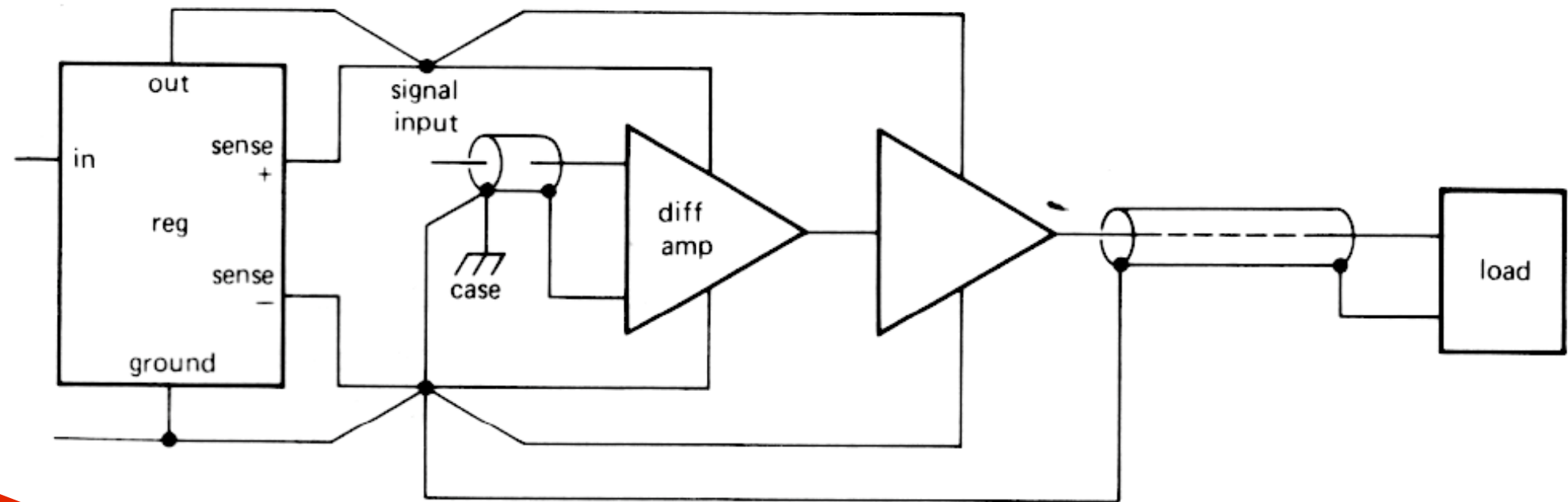





# Filters

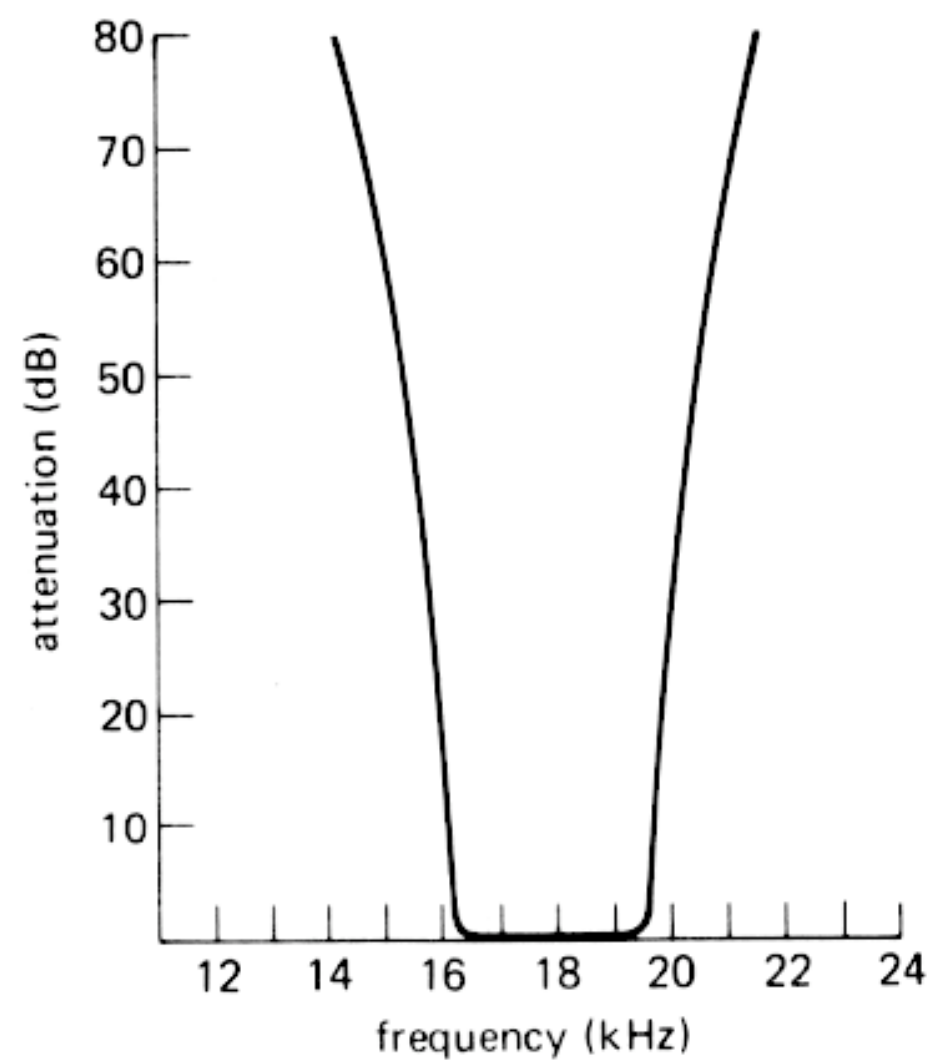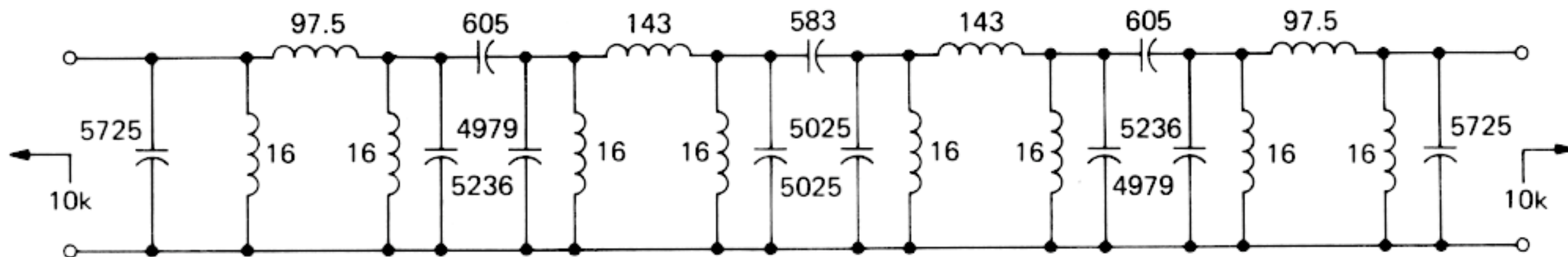


# Shielding

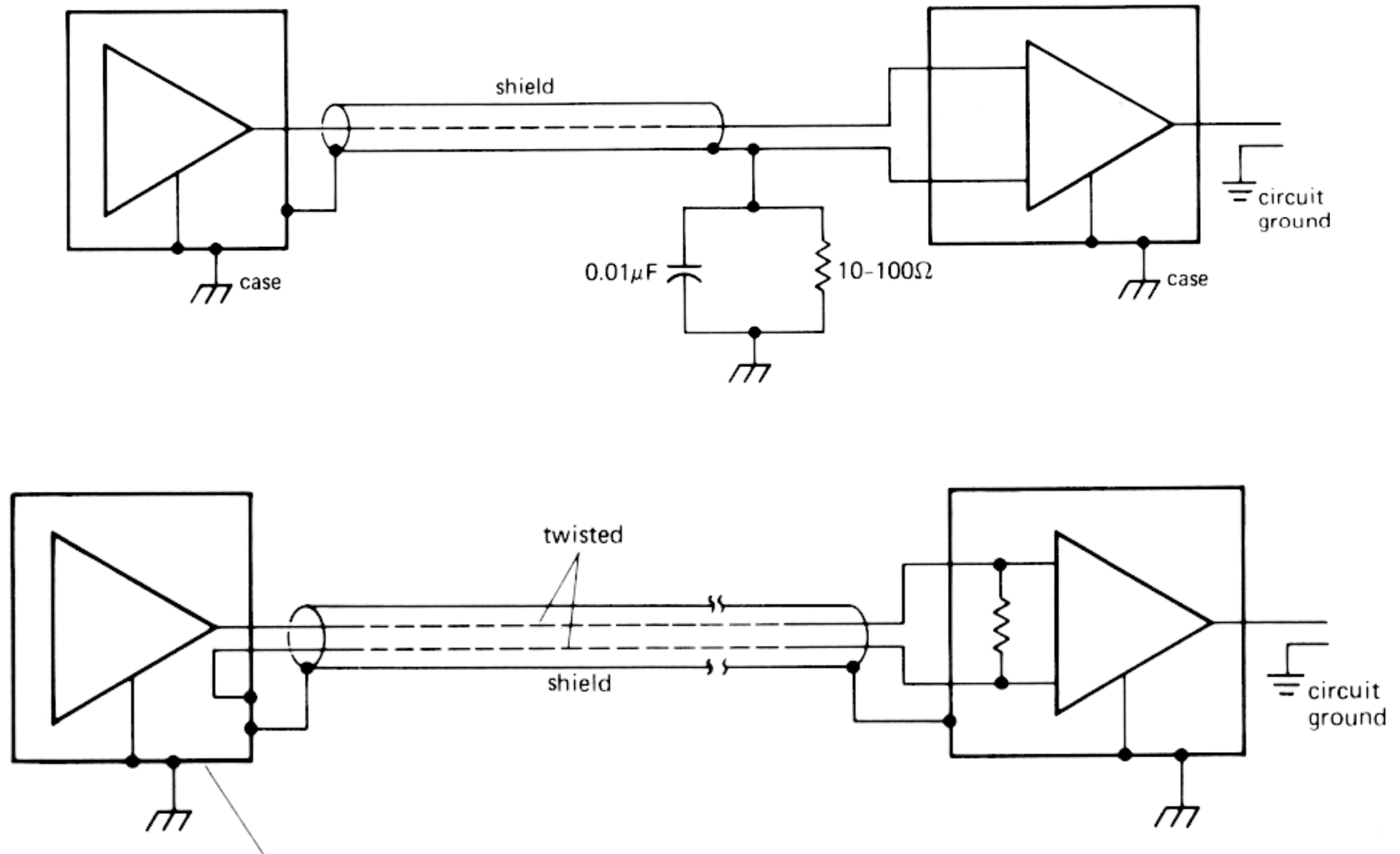

# Noise cancellation

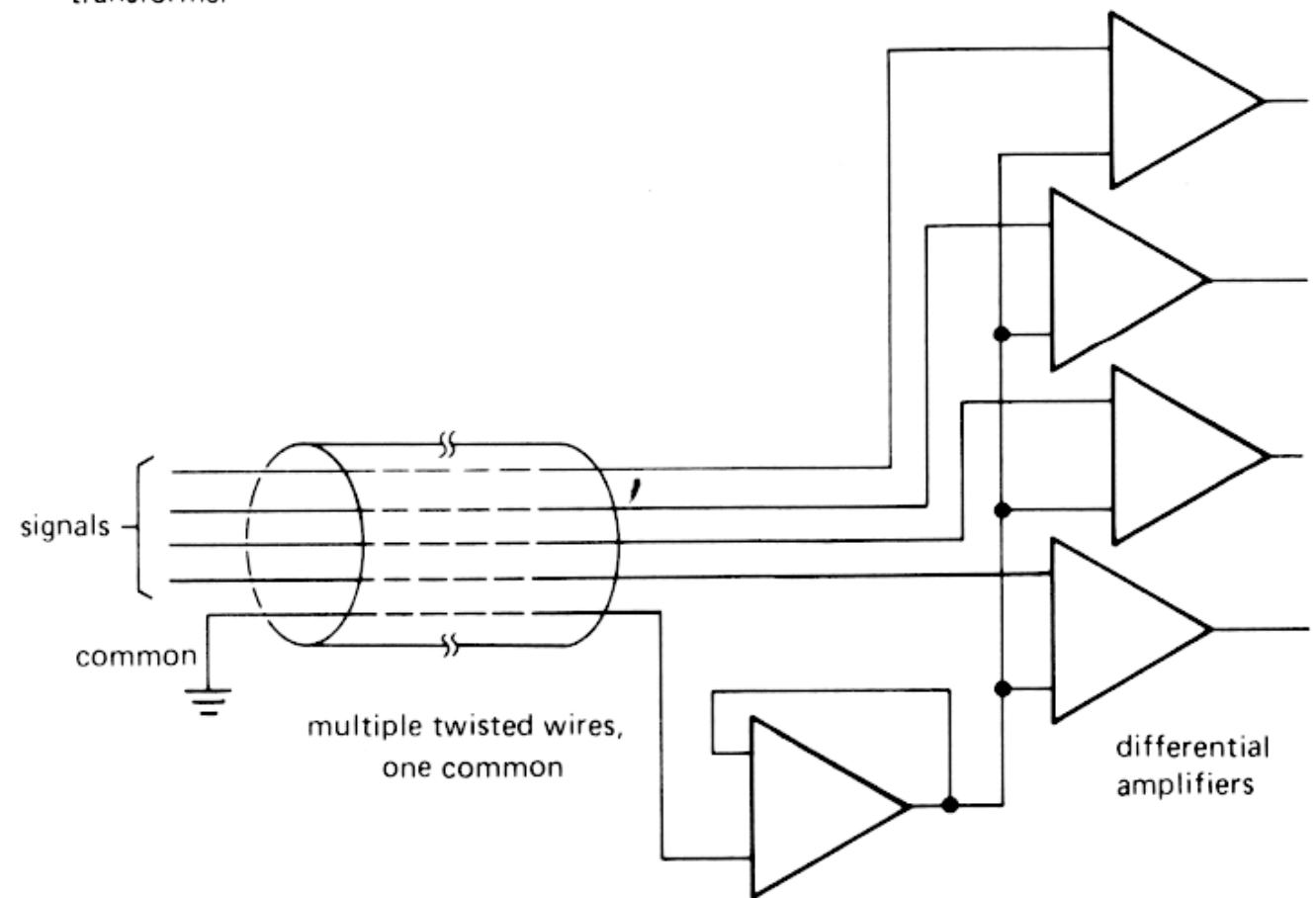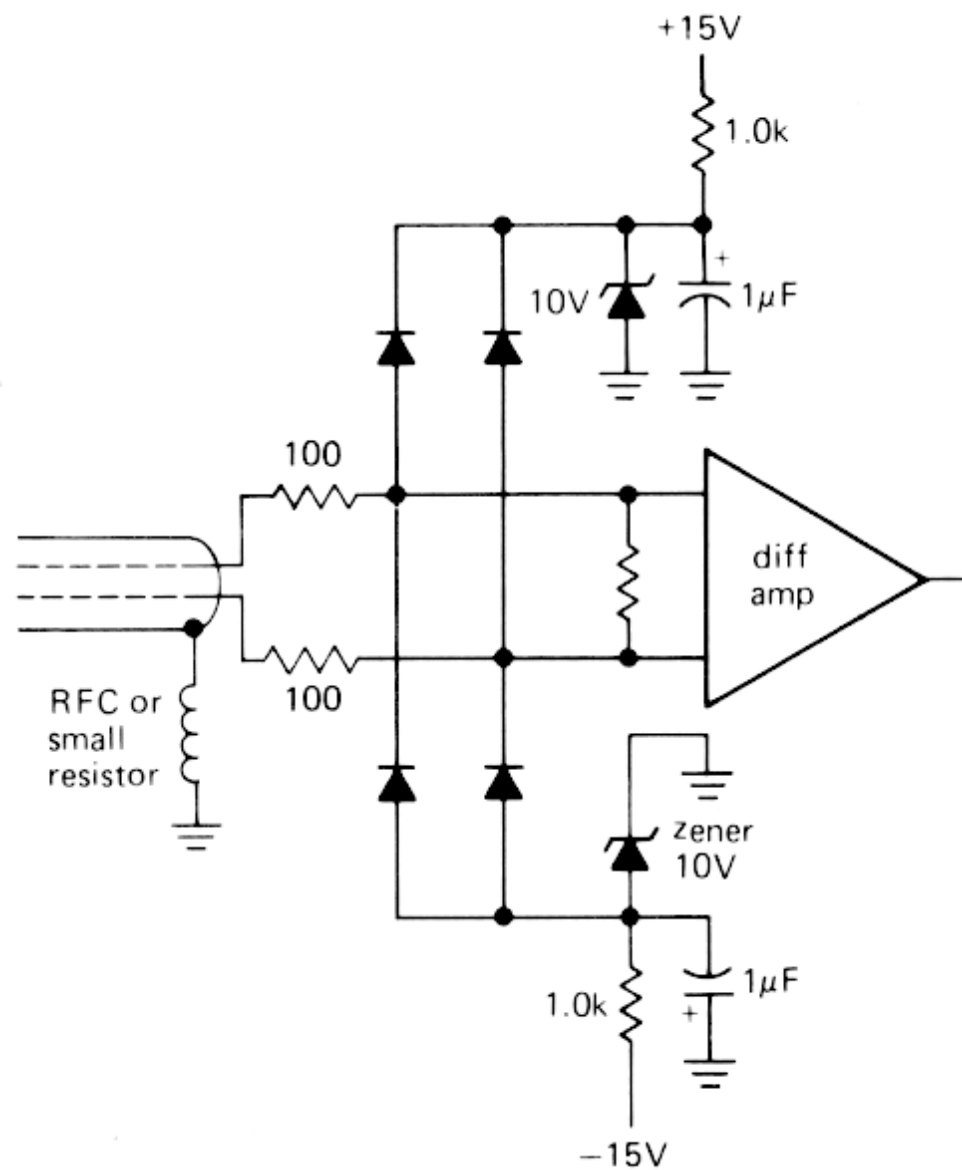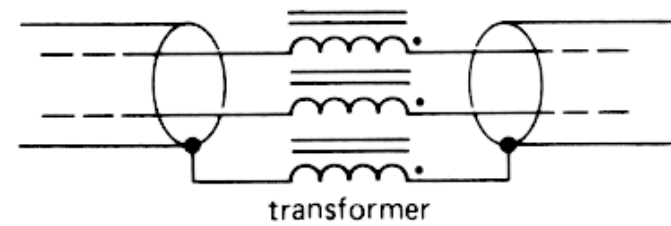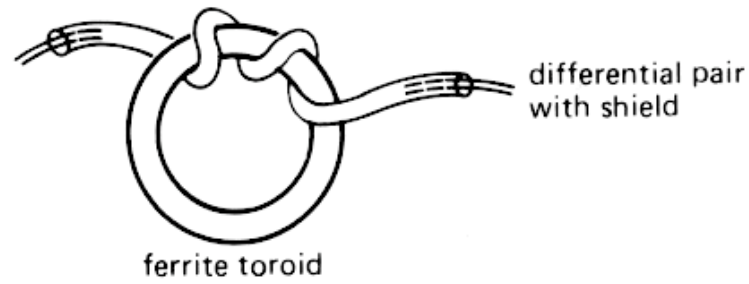

# Lock-in measurements

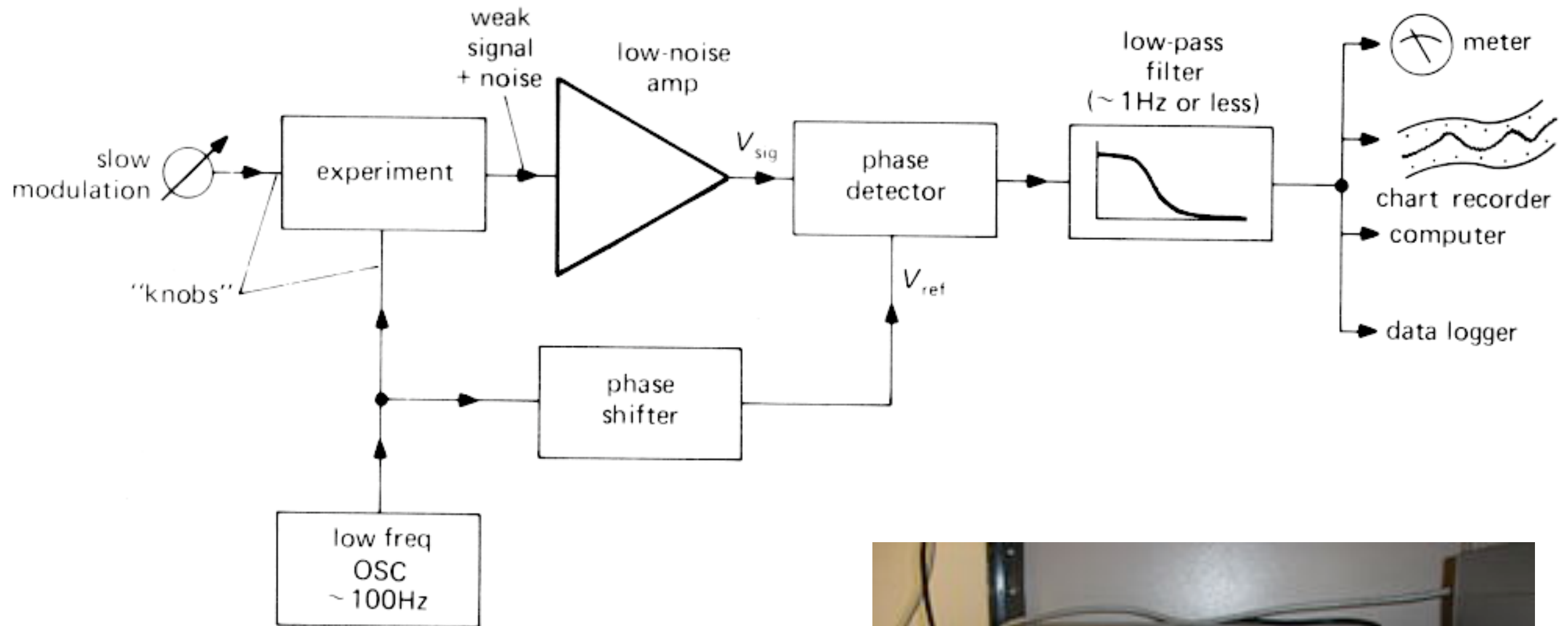

Signal Recovery



Stanford Research Systems